

Digital Logic

Sanjeeb Prasad Panday (Ph.D.)

Assistant Professor

**Department of Electronics and
Computer Engineering , Pulchowk
Campus**

Tribhuvan University



Sequential Logic Counters and Registers

Registers

- Introduction: Registers
 - ❖ Simple Registers
 - ❖ Registers with Parallel Load
- Using Registers to implement Sequential Circuits
- Shift Registers
 - ❖ Serial In/Serial Out Shift Registers
 - ❖ Serial In/Parallel Out Shift Registers
 - ❖ Parallel In/Serial Out Shift Registers
 - ❖ Parallel In/Parallel Out Shift Registers

Sequential Logic Counters and Registers

- Bidirectional Shift Registers
- An Application – Serial Addition

Sequential Logic Counters and Registers

Counters

- Introduction: Counters
- Asynchronous (Ripple) Counters
- Asynchronous Counters with MOD number $< 2^n$
- Asynchronous Down Counters
- Cascading Asynchronous Counters

Sequential Logic Counters and Registers


- Synchronous (Parallel) Counters
- Up/Down Synchronous Counters
- Designing Synchronous Counters
- Decoding A Counter
- Counters with Parallel Load
- Shift Register Counters
 - ❖ Ring Counters
 - ❖ Johnson Counters
- Random-Access Memory (RAM)

Introduction: Registers

- An *n*-bit register has a group of *n* flip-flops and some logic gates and is capable of storing *n* bits of information.
- The flip-flops store the information while the gates control when and how new information is transferred into the register.
- Some functions of register:
 - ❖ retrieve data from register
 - ❖ store/load new data into register (serial or parallel)
 - ❖ shift the data within register (left or right)

Simple Registers

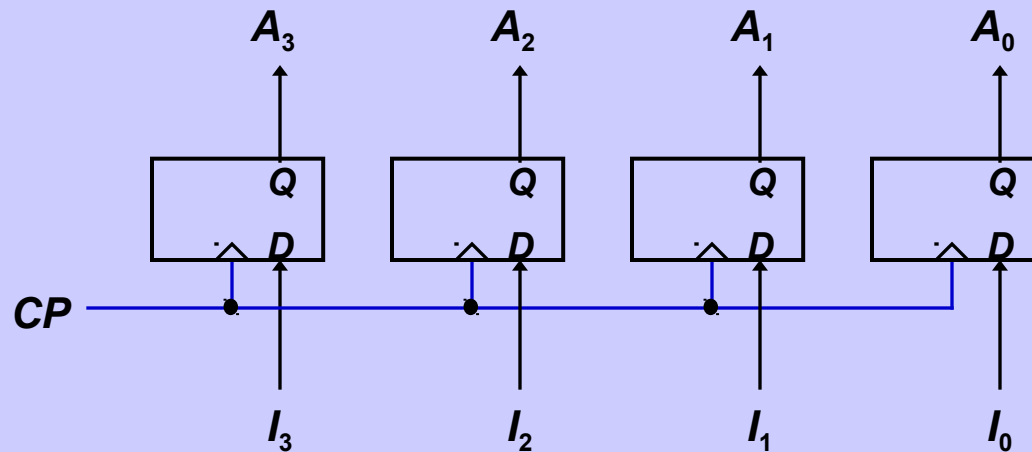
- No external gates.
- Example: A 4-bit register. A new 4-bit data is loaded every clock cycle.



Registers With Parallel Load


- Instead of loading the register at every clock pulse, we may want to control when to load.
- *Loading* a register: transfer new information into the register. Requires a *load* control input.
- *Parallel loading*: all bits are loaded simultaneously.

Registers With Parallel Load

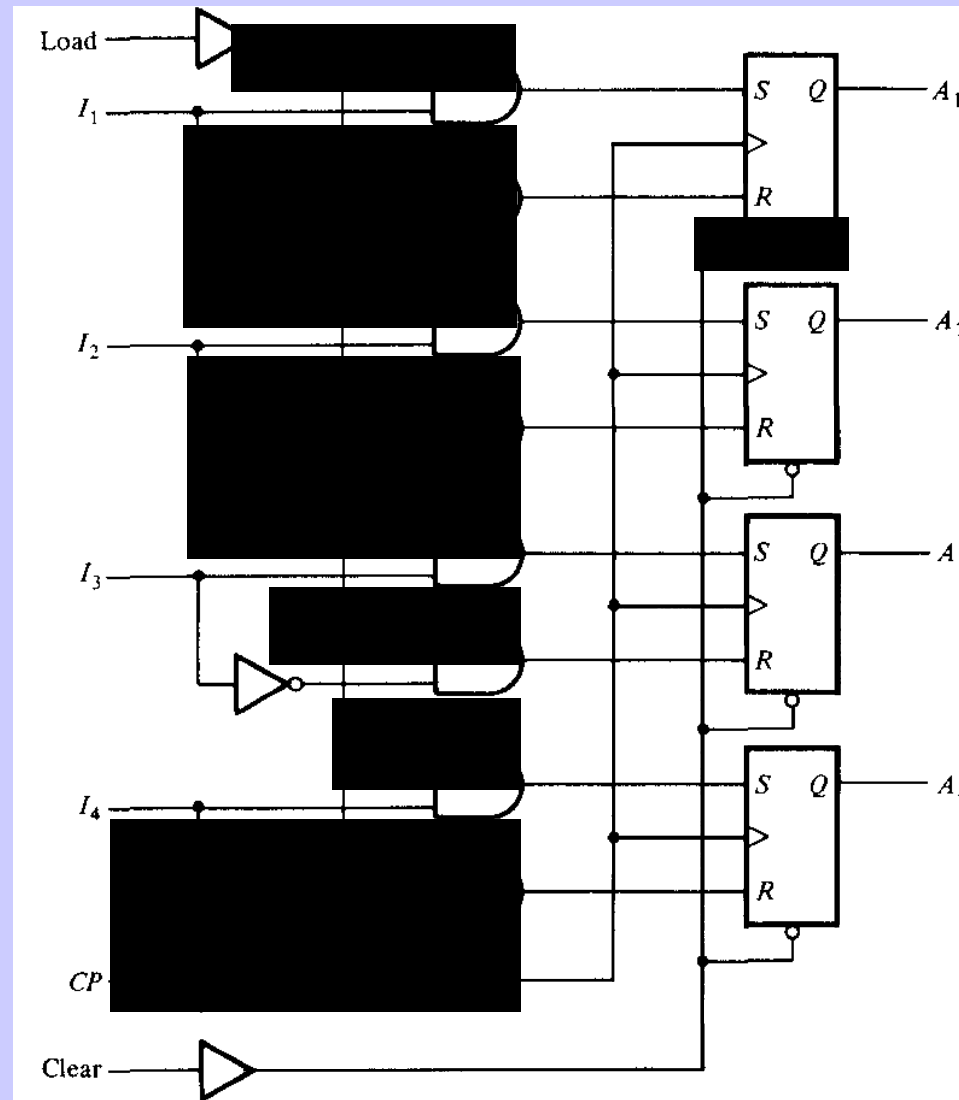


4-bit Register with parallel load

Registers With Parallel Load

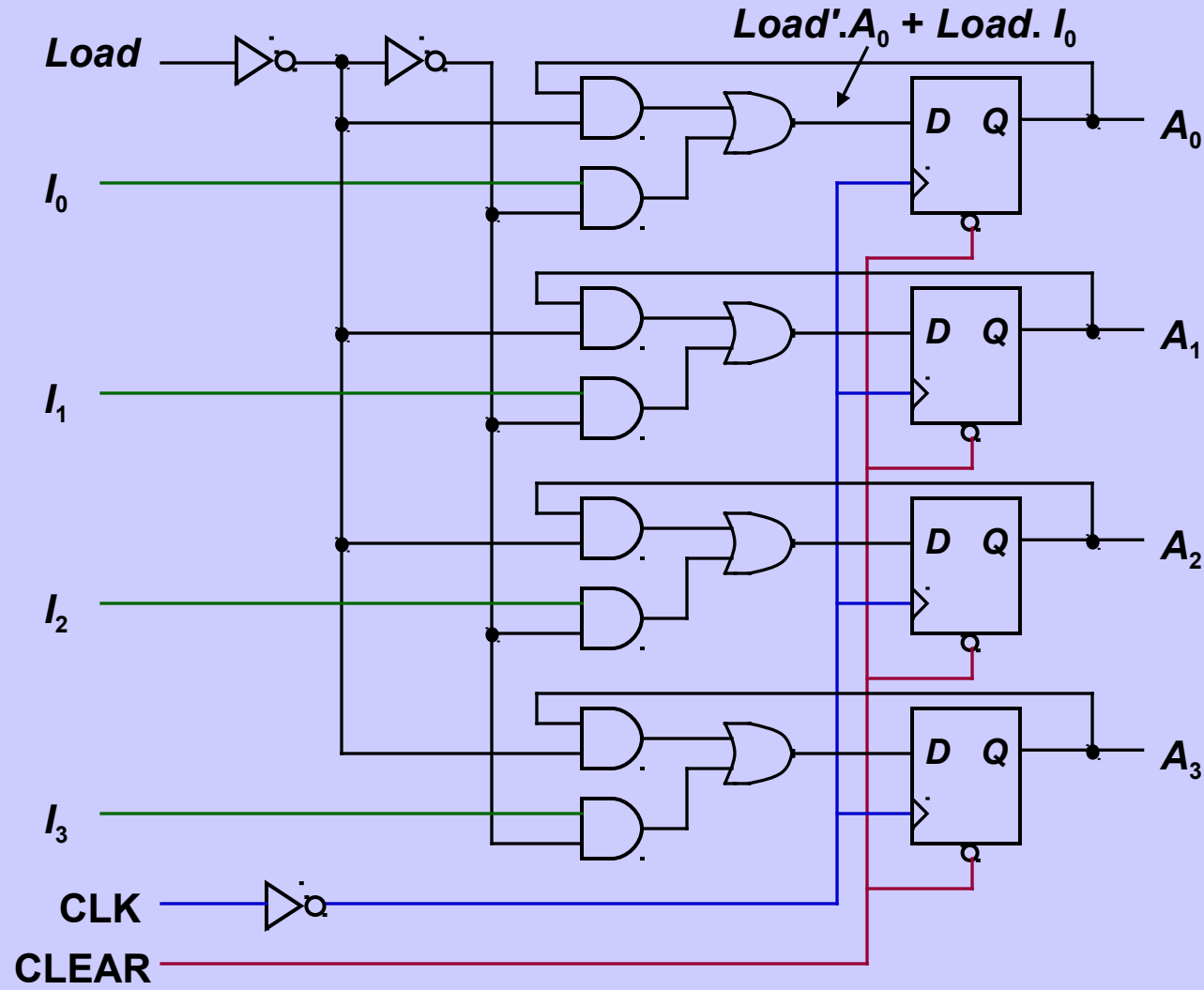

Using Registers to implement Sequential Circuits

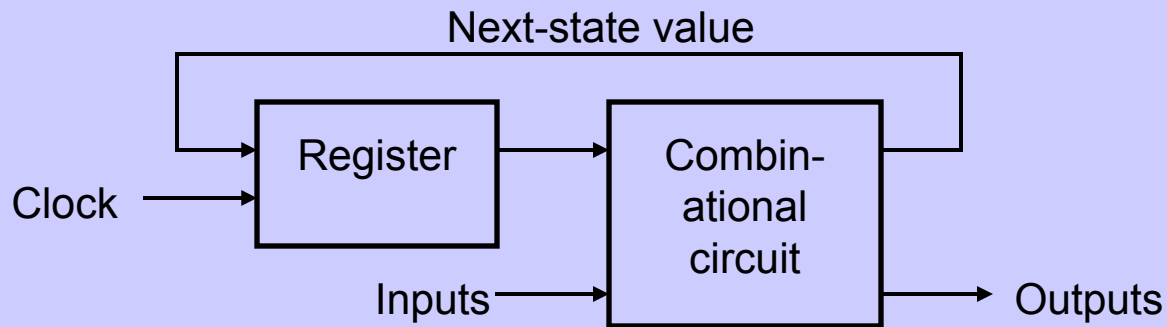- A sequential circuit may consist of a *register* (memory) and a *combinational circuit*.



- The external inputs and present states of the register determine the next states of the register and the external outputs, through the combinational circuit.
- The combinational circuit may be implemented by any of the methods covered in *MSI components* and *Programmable Logic Devices*.

Using Registers to implement Sequential Circuits


■ Example 1:

$$A_1^+ = \sum m(4,6) = A_1 \cdot x'$$

$$A_2^+ = \sum m(1,2,5,6) = A_2 \cdot x' + A_2' \cdot x = A_2 \oplus x$$

$$y = \sum m(3,7) = A_2 \cdot x$$

Present state		Input x	Next State		Output y
A_1	A_2		A_1^+	A_2^+	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1

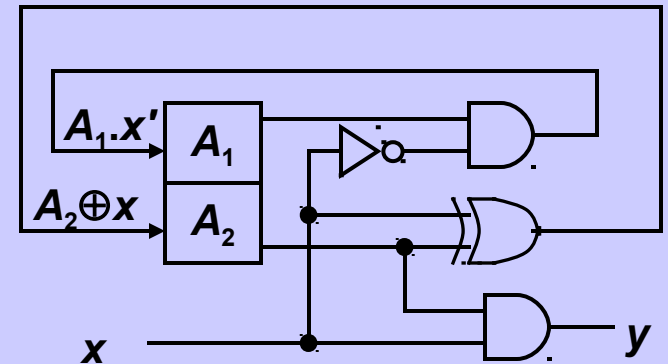


Using Registers to implement Sequential Circuits

- Example 2: Repeat example 1, but use a ROM.

Address			Outputs		
1	2	3	1	2	3
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1

ROM truth table

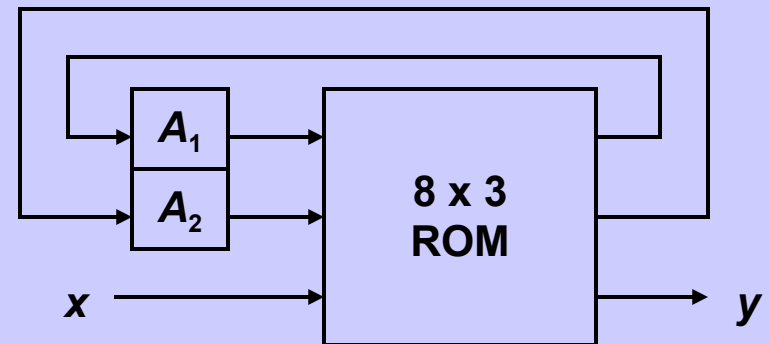


Shift Registers

- Another function of a register, besides storage, is to provide for *data movements*.
- Each *stage* (flip-flop) in a shift register represents one bit of storage, and the shifting capability of a register permits the movement of data from stage to stage within the register, or into or out of the register upon application of clock pulses.




Shift Registers

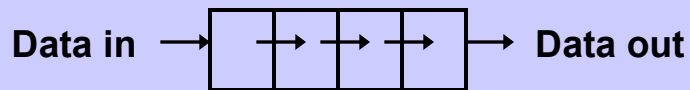
- Basic data movement in shift registers (four bits are used for illustration).




(a) Serial in/shift right/serial out

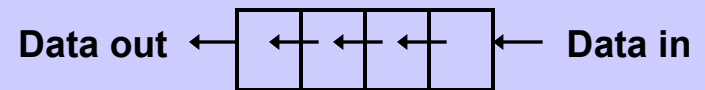


(b) Serial in/shift left/serial out

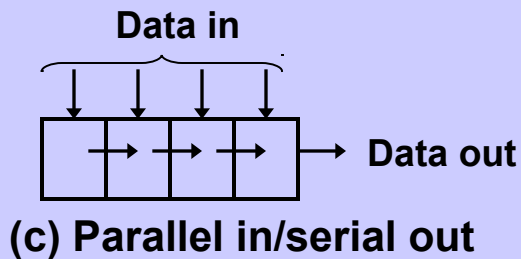


(c) Parallel in/serial out

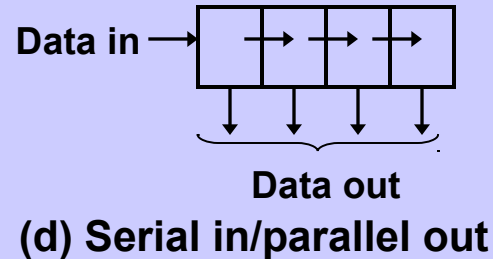


(d) Serial in/parallel out

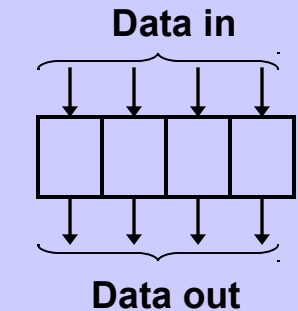

(e) Parallel in / parallel out

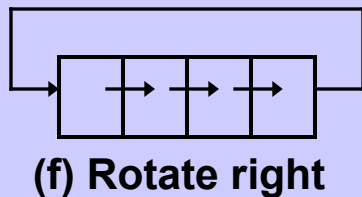


(f) Rotate right

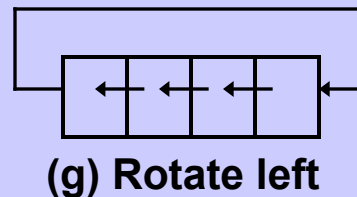

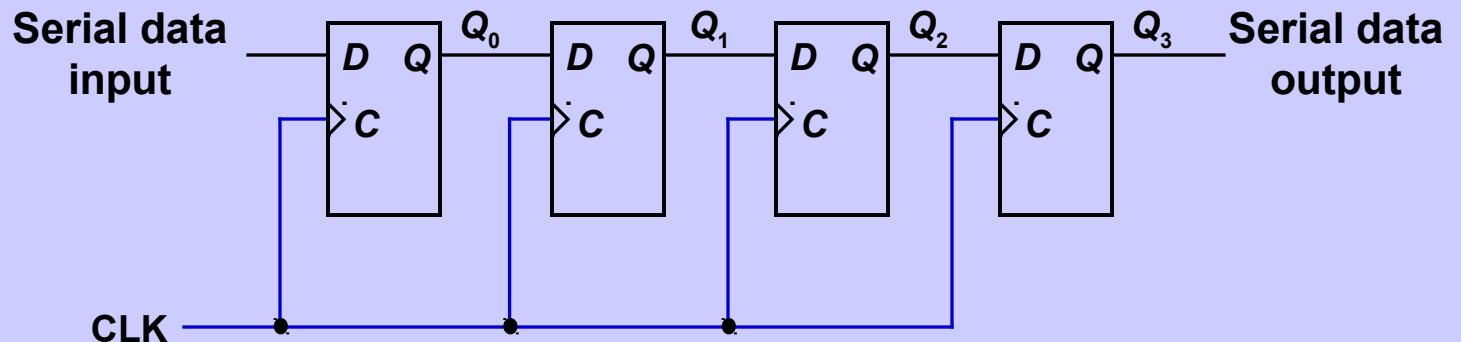(g) Rotate left


Serial In/Serial Out Shift Registers

- Accepts data serially – one bit at a time – and also produces output serially.



Serial In/Serial Out Shift Registers

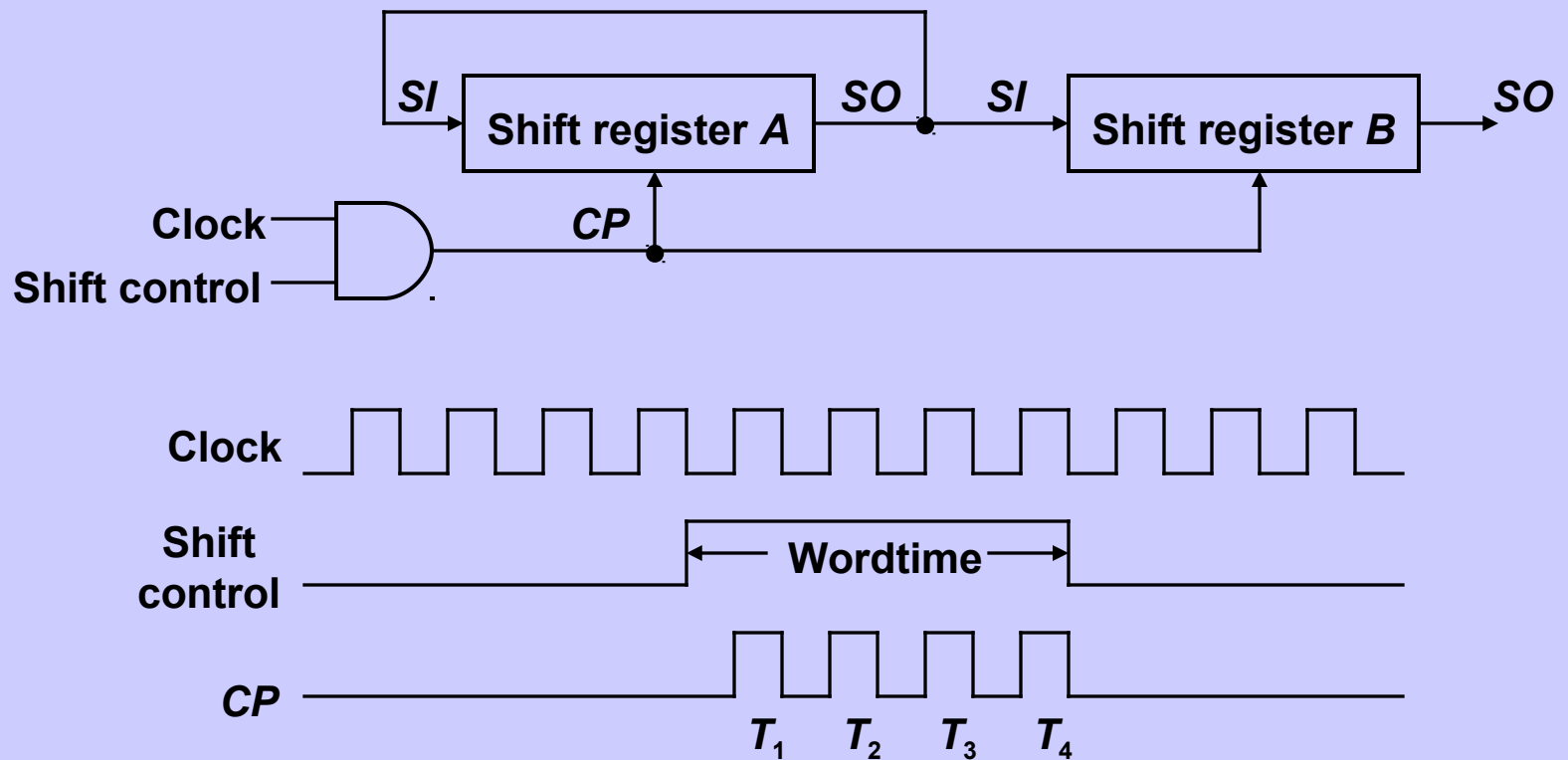- Application: Serial transfer of data from one register to another.





Serial In/Serial Out Shift Registers

- Serial-transfer example.

Timing Pulse	Shift register A	Shift register B	Serial output of B
Initial value	1 0 1 1	0 0 1 0	0
After T_1	1 1 0 1	1 0 0 1	1
After T_2	1 1 1 0	1 1 0 0	0
After T_3	0 1 1 1	0 1 1 0	0
After T_4	1 0 1 1	1 0 1 1	1


Serial In/Parallel Out Shift Registers

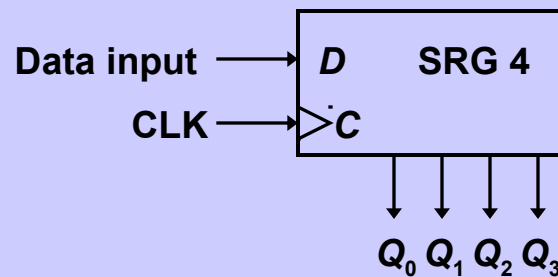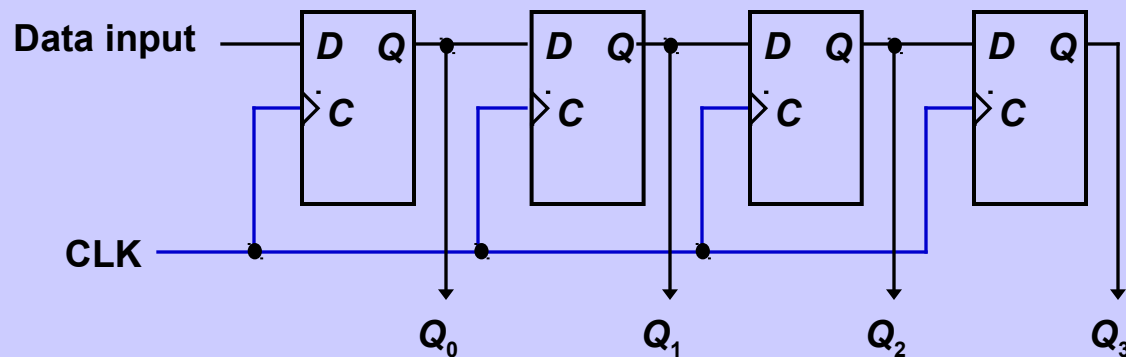- Accepts data serially.
- Outputs of all stages are available simultaneously.




Logic symbol

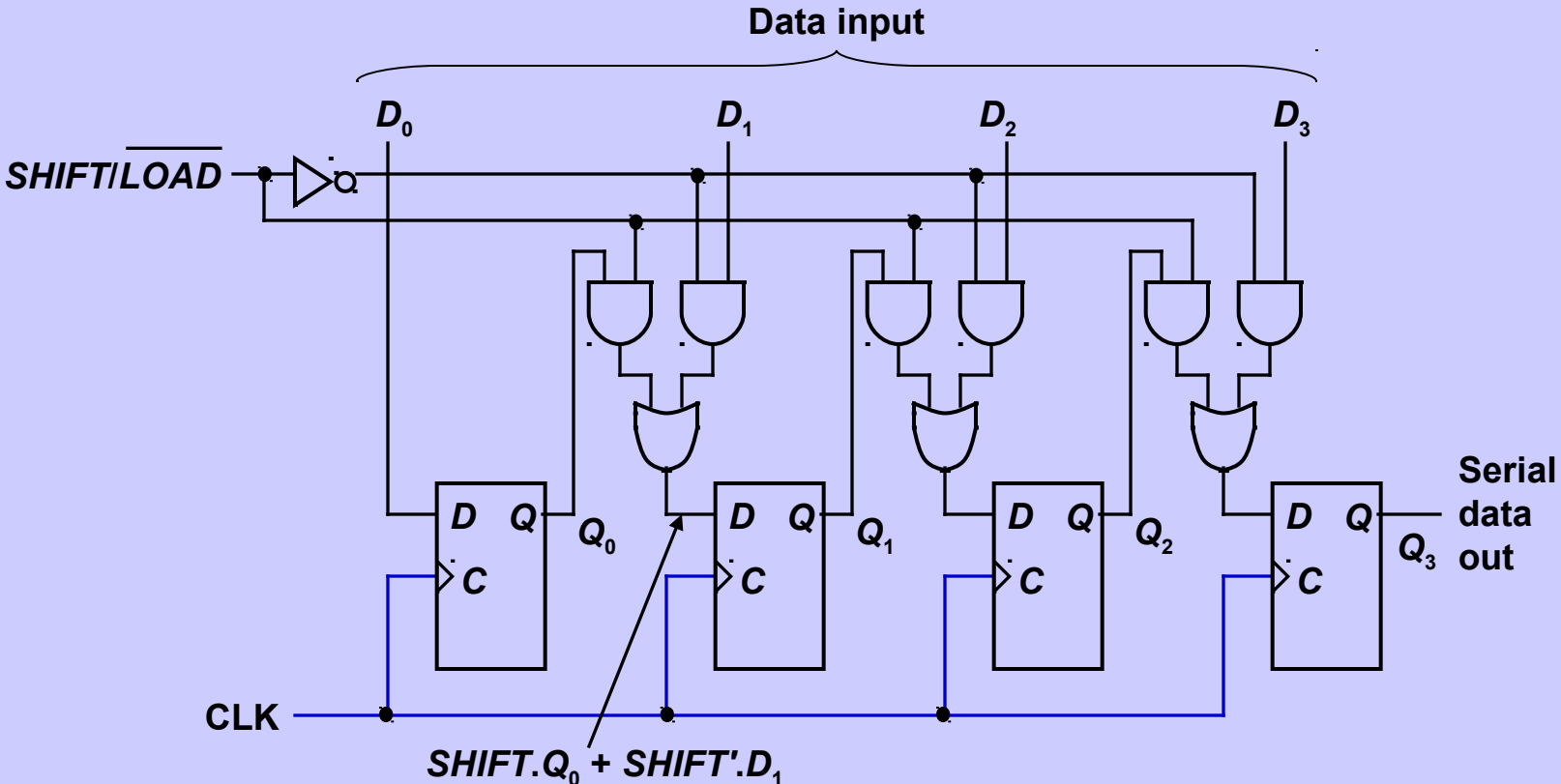- Bits are entered simultaneously, but output is serial.



Parallel In/Serial Out Shift Registers

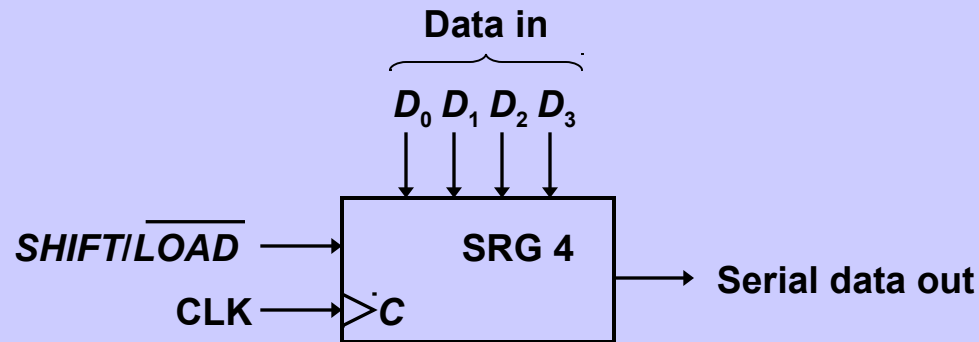
- Bits are entered simultaneously, but output is serial.



Logic symbol


Parallel In/Parallel Out Shift Registers

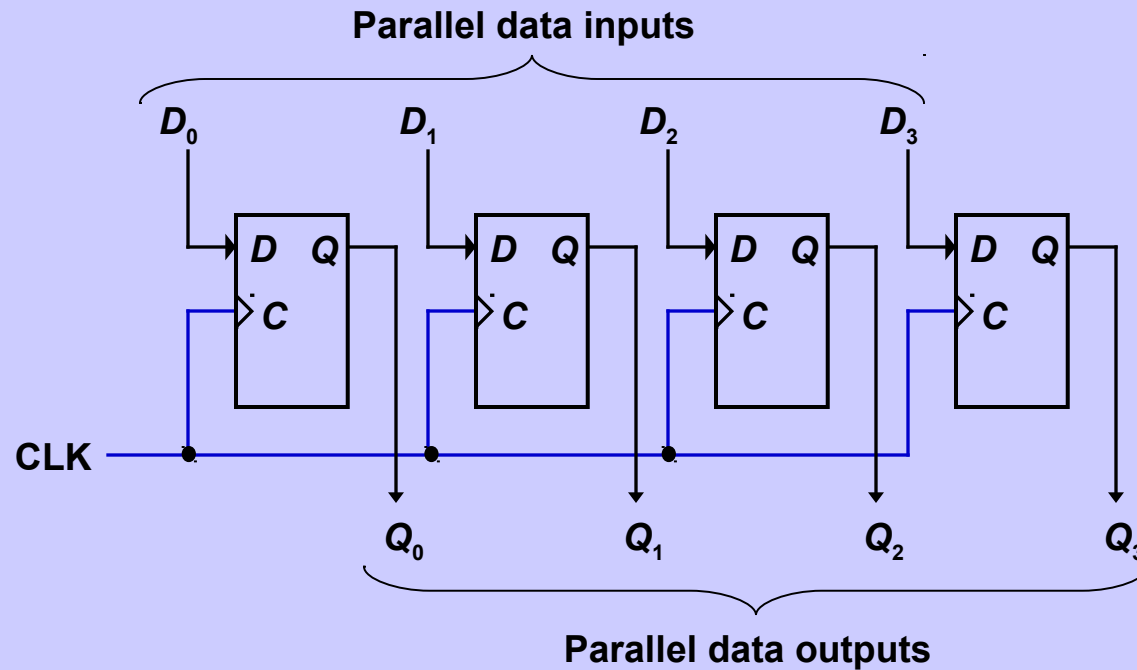- Simultaneous input and output of all data bits.




Bidirectional Shift Registers

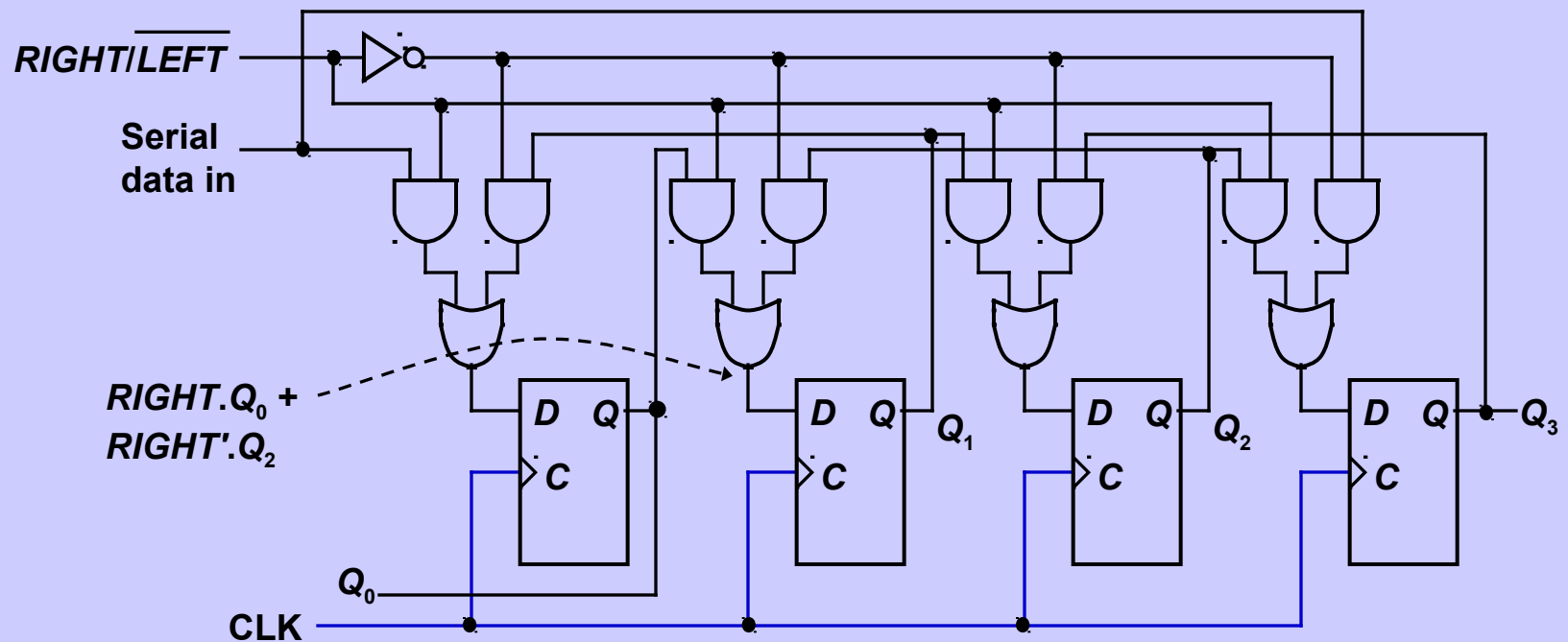- Data can be shifted either left or right, using a control line $\overline{RIGHT/LEFT}$ (or simply $RIGHT$) to indicate the direction.



Bidirectional Shift Registers

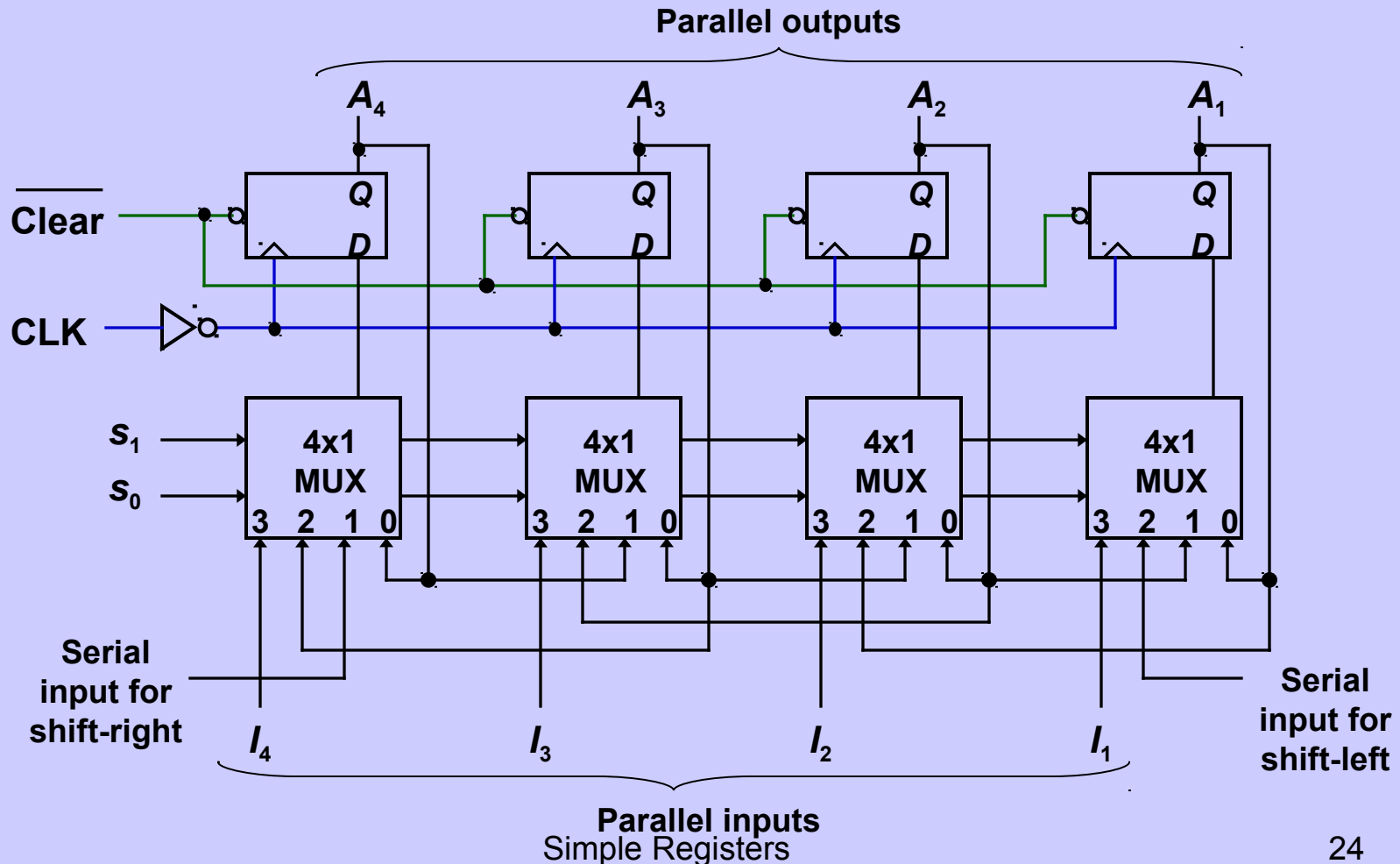- 4-bit bidirectional shift register with parallel load.




Bidirectional Shift Registers

- 4-bit bidirectional shift register with parallel load.

<i>Mode Control</i>		<i>Register Operation</i>
s_1	s_0	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

An Application – Serial Addition

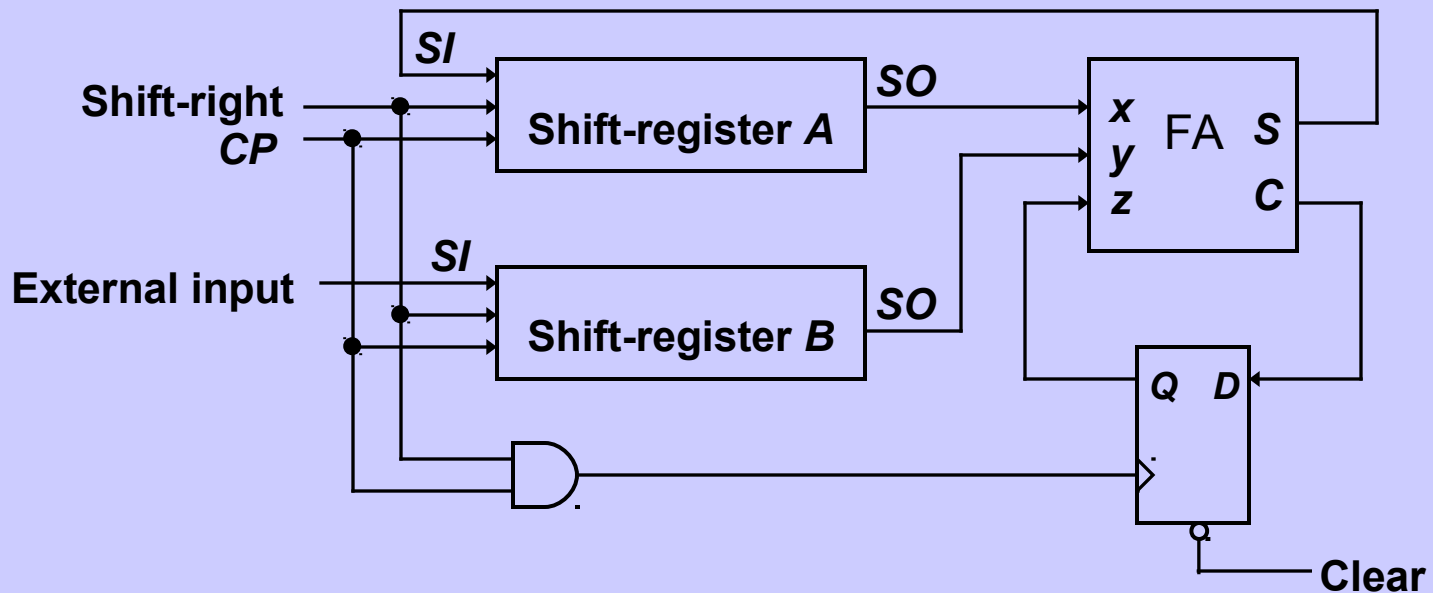- Most operations in digital computers are done in parallel. Serial operations are slower but require less equipment.
- A serial adder is shown below. $A \leftarrow A + B$.



Serial Adder

. These functions are specified in the excitation table and can be simplified maps:

$$JQ = xy$$

$$KQ = x'y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

As shown in Fig. 7-11, the circuit consists of three gates and a *JK* flip-flop. Shift registers are also included in the diagram to show the complete serial adder. The output *S* is a function not only of *x* and *y*, but also of the present state of the flip-flop. The next state of *Q* is a function of the present values of *x* and *y* that come out of the shift registers.

$$JQ = xy$$

$$KQ = x'y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

Serial Adder

TABLE 7-3
Excitation Table for a Serial Adder

Present State	Inputs		Next State	Output	Flip-Flop Inputs	
	x	y	Q	S	JQ	KQ
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X

An Application – Serial Addition

- $A = 0100$; $B = 0111$. $A + B = 1011$ is stored in A after 4 clock pulses.

Initial:	A: 0 1 0 0 B: 0 1 1 1	Q: 0
Step 1: $0 + 1 + 0$ S = 1, C = 0	A: 1 0 1 0 B: x 0 1 1	Q: 0
Step 2: $0 + 1 + 0$ S = 1, C = 0	A: 1 1 0 1 B: x x 0 1	Q: 0
Step 3: $1 + 1 + 0$ S = 0, C = 1	A: 0 1 1 0 B: x x x 0	Q: 1
Step 4: $0 + 0 + 1$ S = 1, C = 0	A: 1 0 1 1 B: x x x x	Q: 0

Introduction: Counters



- **Counters** are circuits that cycle through a specified number of states.
- Two types of counters:
 - ❖ synchronous (parallel) counters
 - ❖ asynchronous (ripple) counters
- Ripple counters allow some flip-flop outputs to be used as a source of clock for other flip-flops.
- Synchronous counters apply the same clock to all flip-flops.

Asynchronous (Ripple) Counters

- **Asynchronous counters**: the flip-flops do not change states at exactly the same time as they do not have a common clock pulse.
- Also known as **ripple counters**, as the input clock pulse “ripples” through the counter – cumulative delay is a drawback.
- n flip-flops \rightarrow a MOD (modulus) 2^n counter. (Note: A MOD- x counter cycles through x states.)
- Output of the last flip-flop (MSB) divides the input clock frequency by the MOD number of the counter, hence a counter is also a *frequency divider*.

Asynchronous (Ripple) Counters

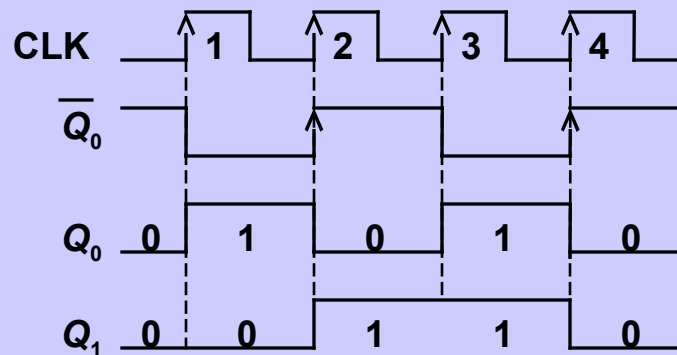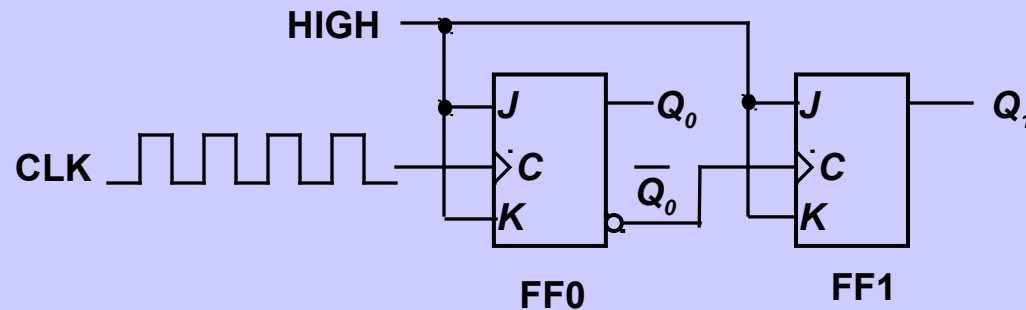- Example: 2-bit ripple binary counter.
- Output of one flip-flop is connected to the clock input of the next more-significant flip-flop.




Timing diagram

00 → 01 → 10 → 11 → 00 ...


Asynchronous (Ripple) Counters

- Example: 3-bit ripple binary counter.

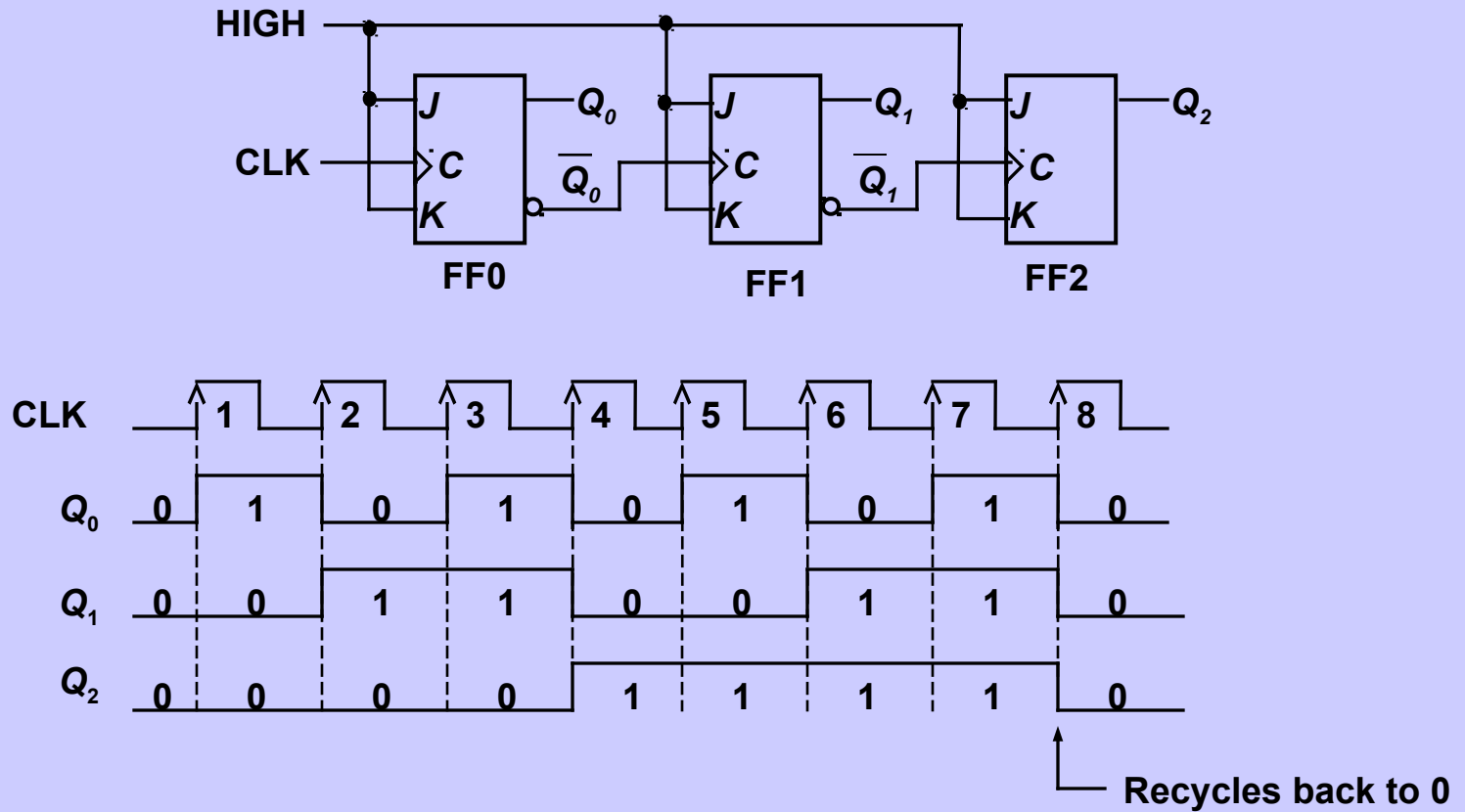



Asynchronous (Ripple) Counters

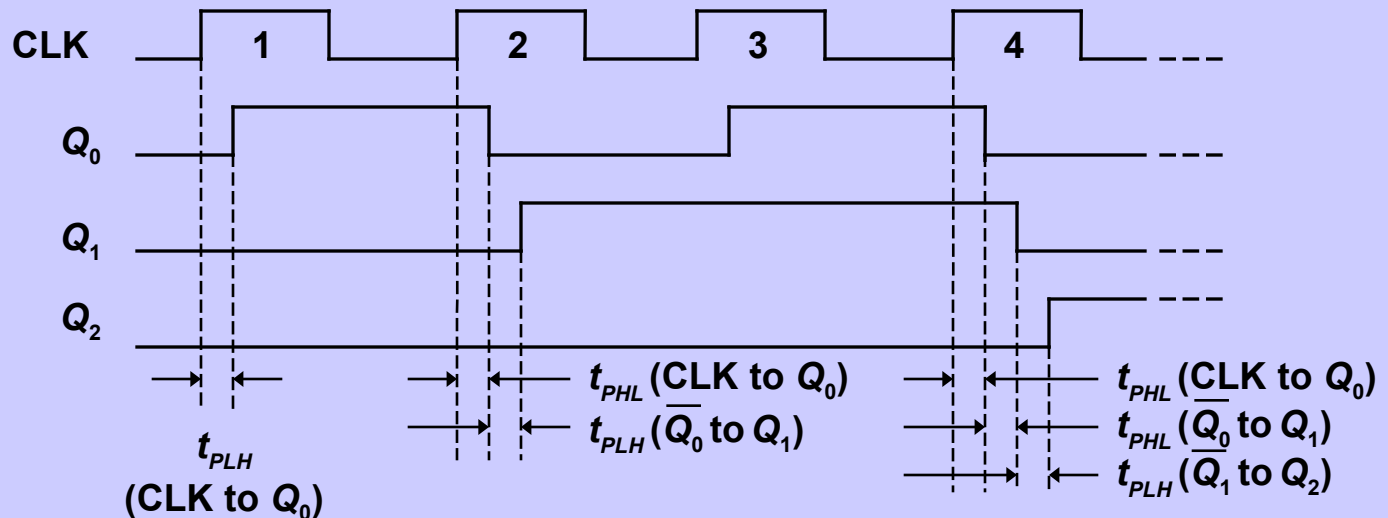- Propagation delays in an asynchronous (ripple-clocked) binary counter.
- If the accumulated delay is greater than the clock pulse, some counter states may be misrepresented!



Asynchronous (Ripple) Counters

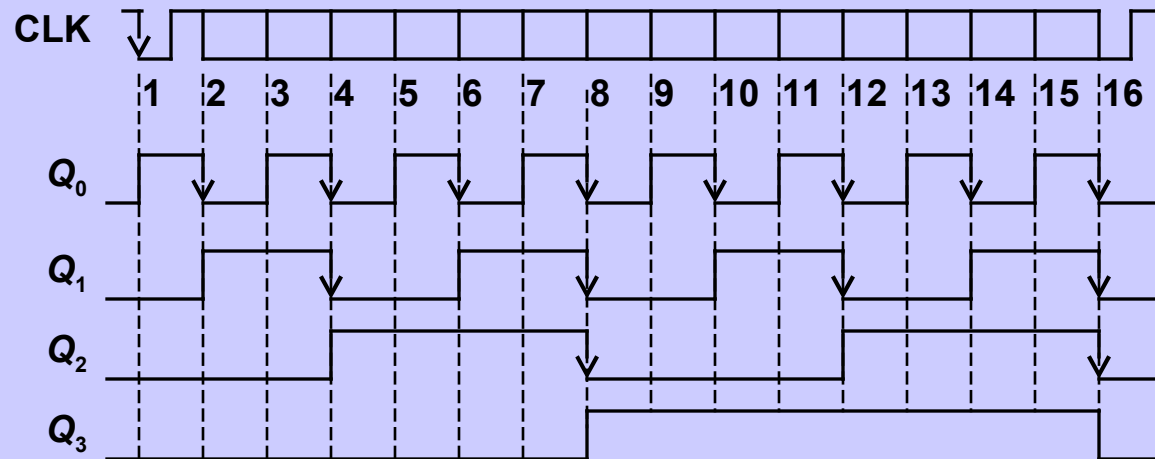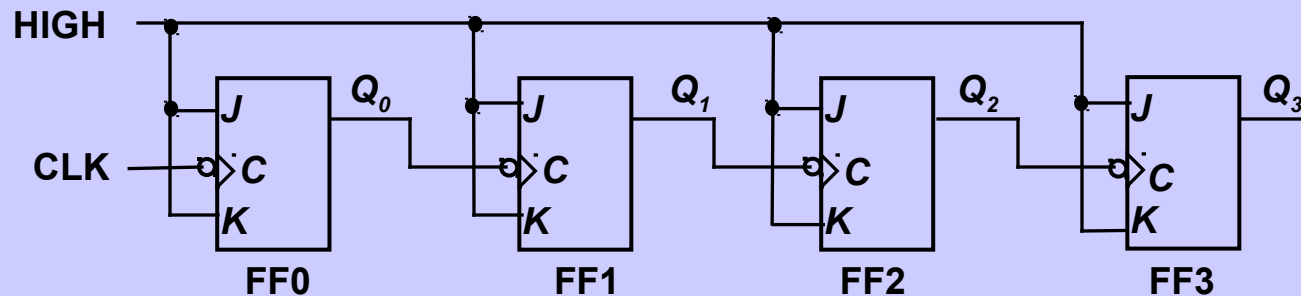
- Example: 4-bit ripple binary counter (negative-edge triggered).



Asyn. Counters with MOD no. $< 2^n$



- States may be skipped resulting in a **truncated sequence**.
- Technique: force counter to *recycle before going through all of the states* in the binary sequence.
- Example: Given the following circuit, determine the counting sequence (and hence the modulus no.)

All J, K inputs are 1 (HIGH).

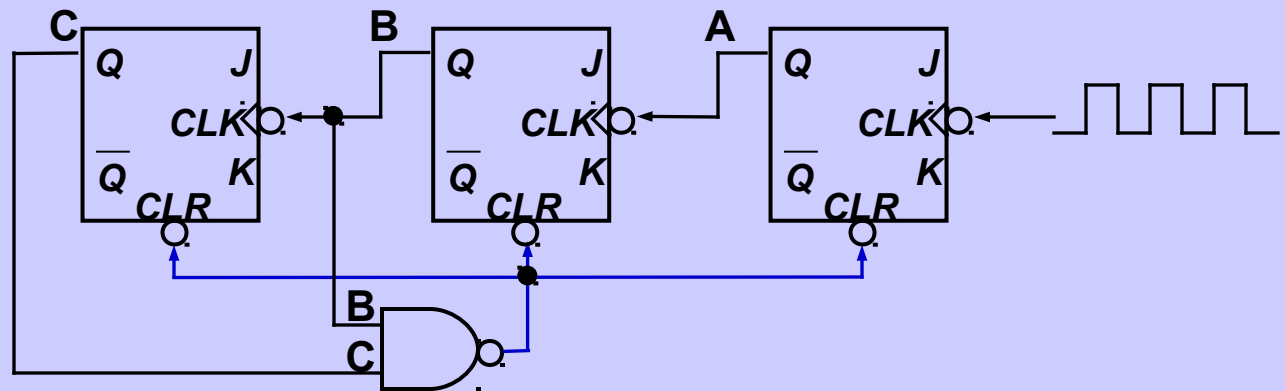



Asyn. Counters with MOD no. $< 2^n$

- Example (cont'd):

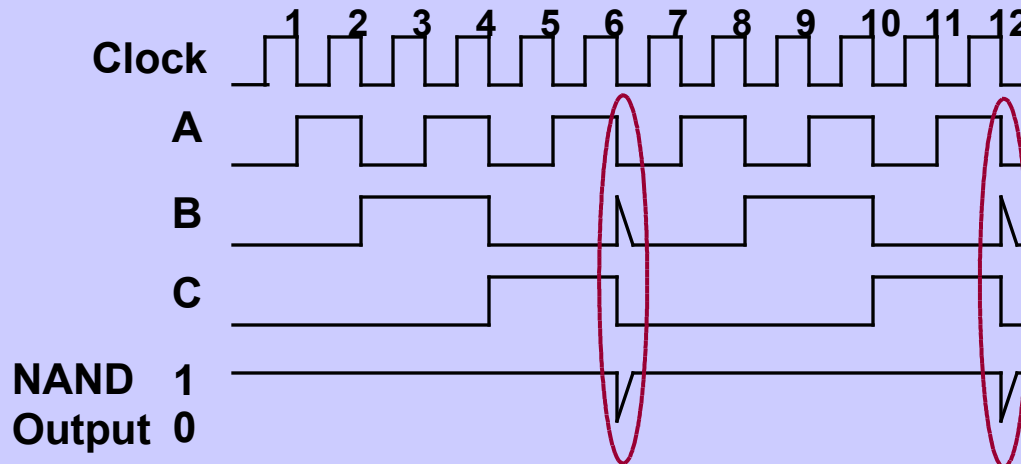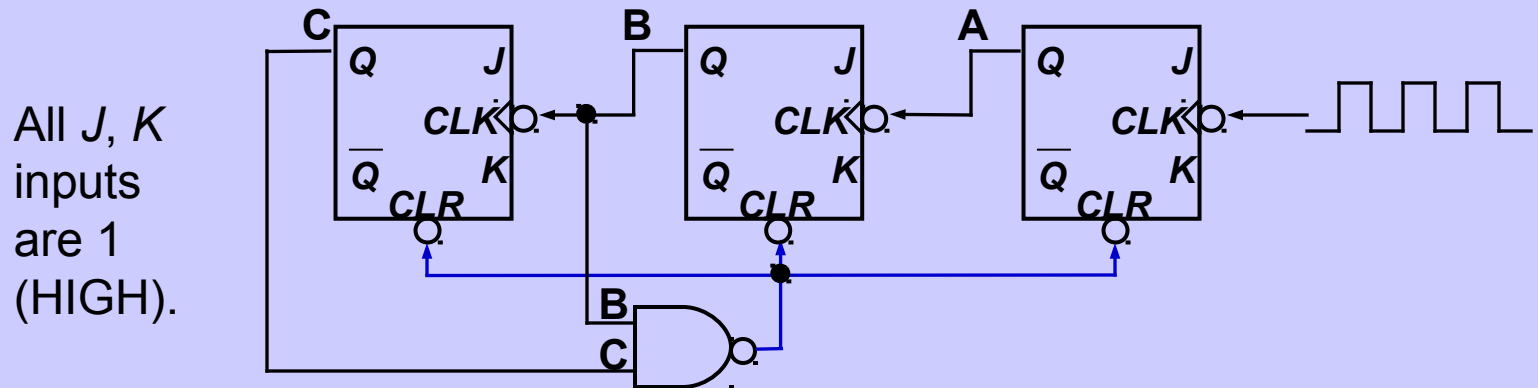

MOD-6 counter
produced by
clearing (a MOD-8
binary counter)
when count of six
(110) occurs.

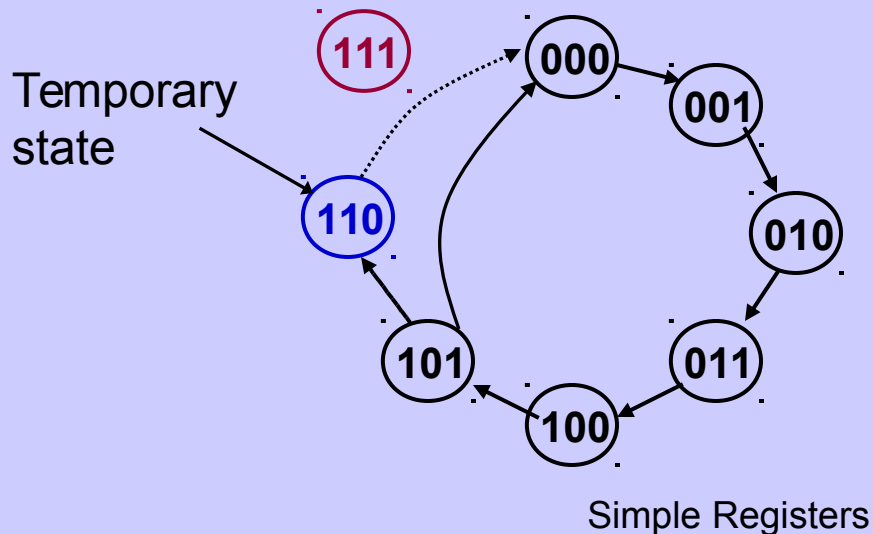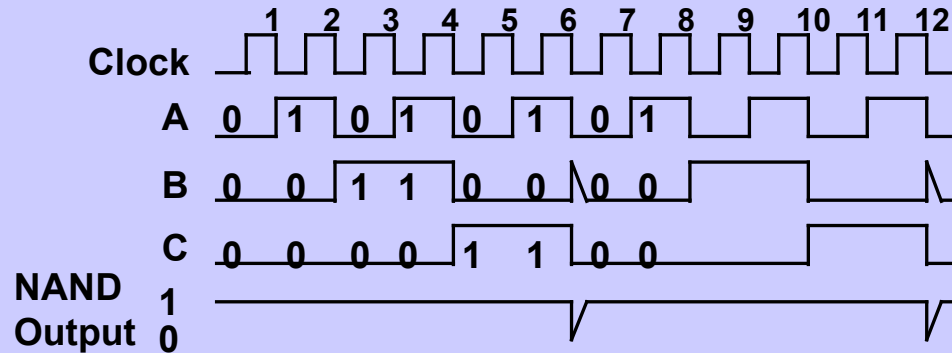
- Example (cont'd): Counting sequence of circuit (in CBA order).



Counter is a MOD-6 counter.


Asyn. Counters with MOD no. $< 2^n$

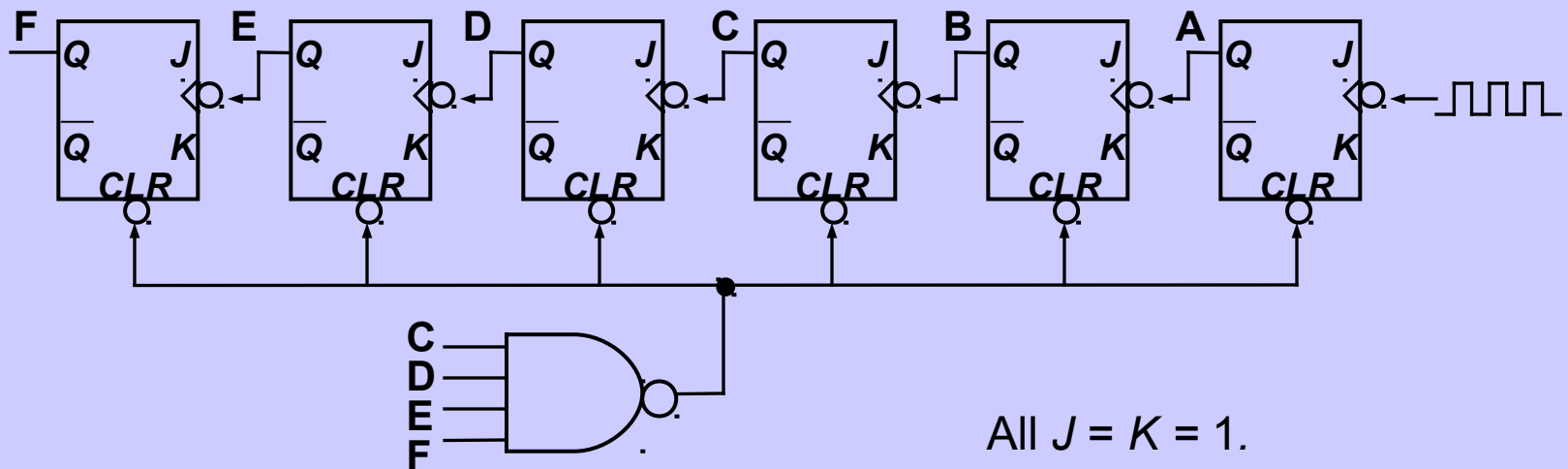- *Exercise:* How to construct an asynchronous MOD-5 counter? MOD-7 counter? MOD-12 counter?
- *Question:* The following is a MOD-? counter?





Asyn. Counters with MOD no. $< 2^n$

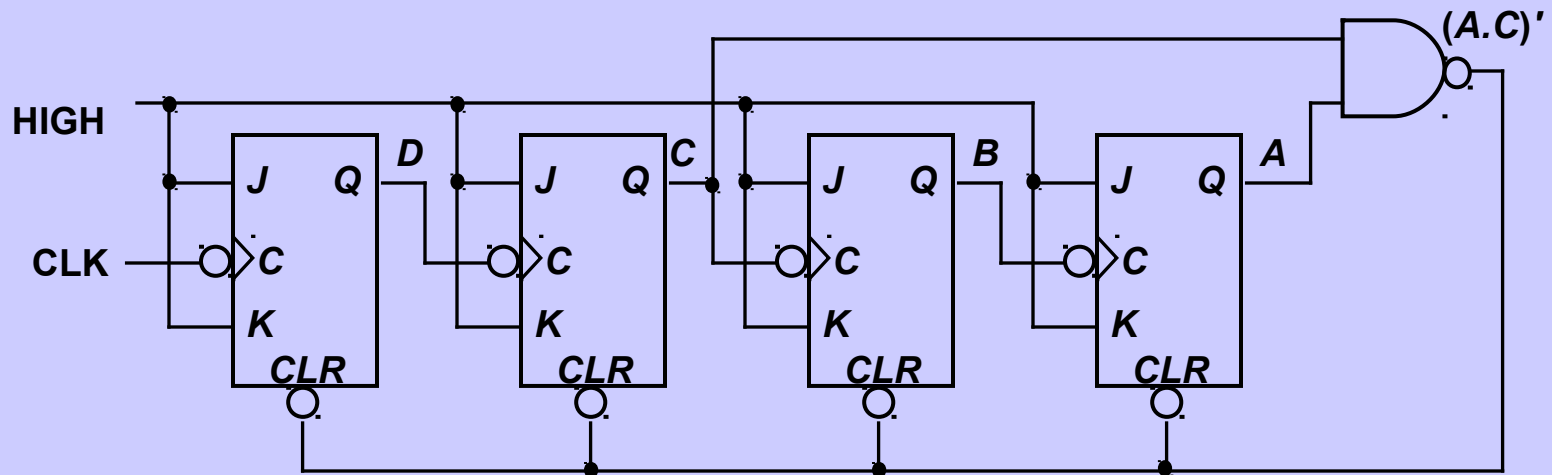- **Decade counters** (or **BCD counters**) are counters with 10 states (modulus-10) in their sequence. They are commonly used in daily life (e.g.: utility meters, odometers, etc.).
- Design an asynchronous decade counter.




Asyn. Counters with MOD no. $< 2^n$

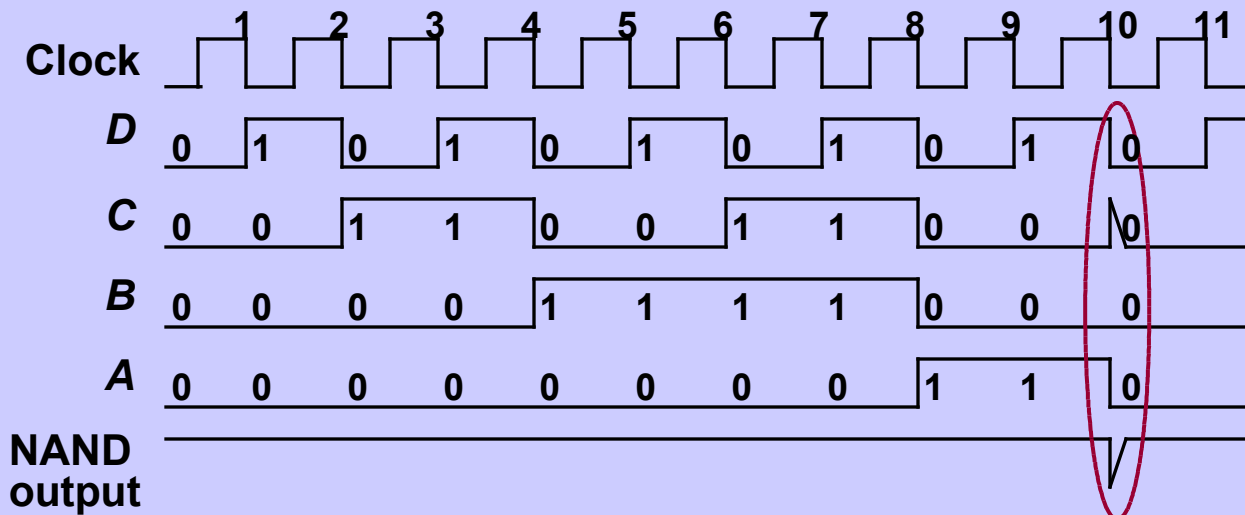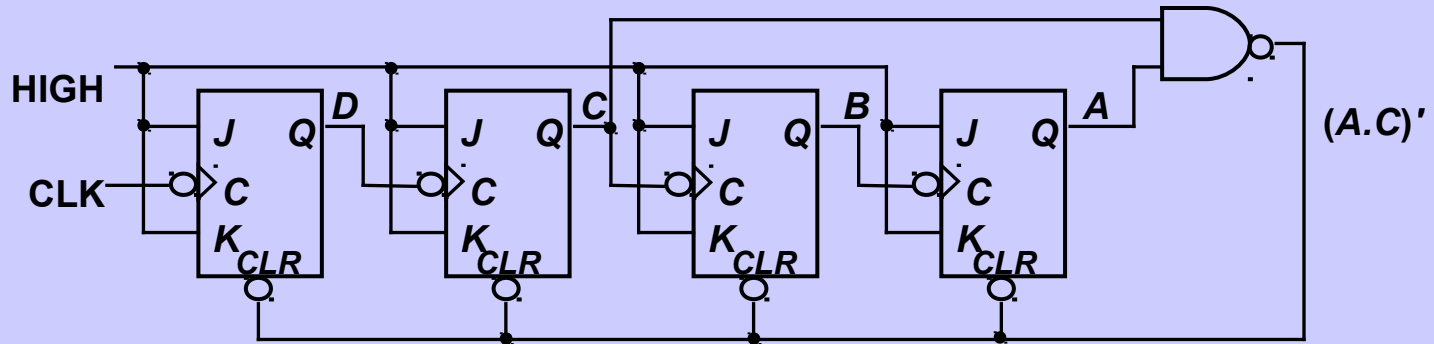- Asynchronous decade/BCD counter (cont'd).




Asynchronous Down Counters

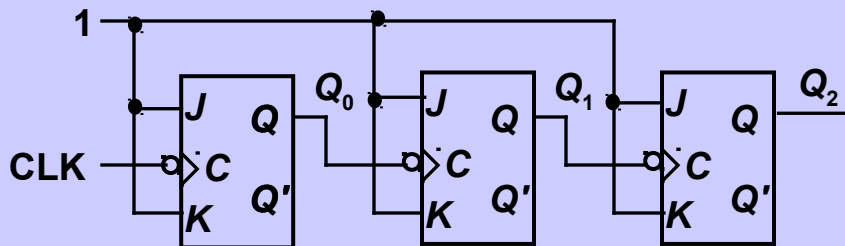- So far we are dealing with *up counters*. *Down counters*, on the other hand, count downward from a maximum value to zero, and repeat.
- Example: A 3-bit binary (MOD-2³) down counter.




3-bit binary
up counter

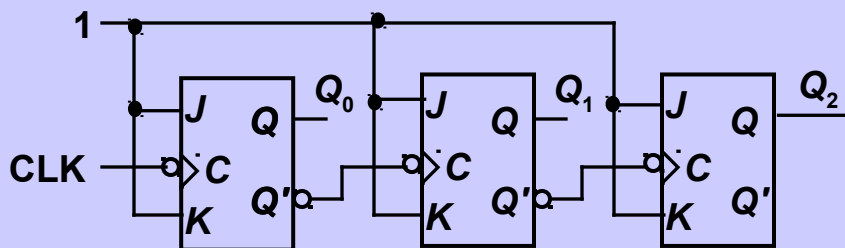

3-bit binary
down counter


Asynchronous Down Counters

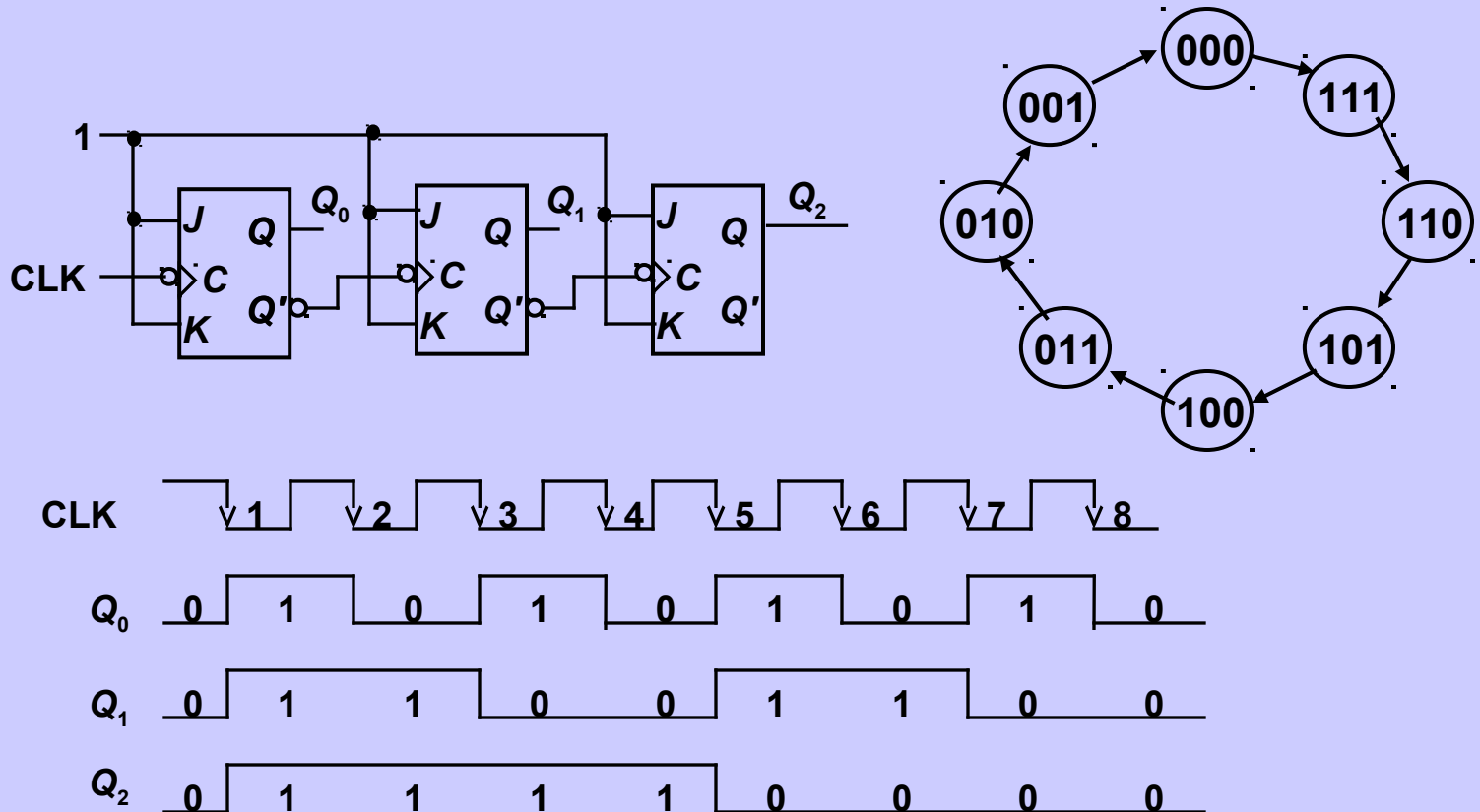- Example: A 3-bit binary (MOD-8) down counter.




Cascading Asynchronous Counters

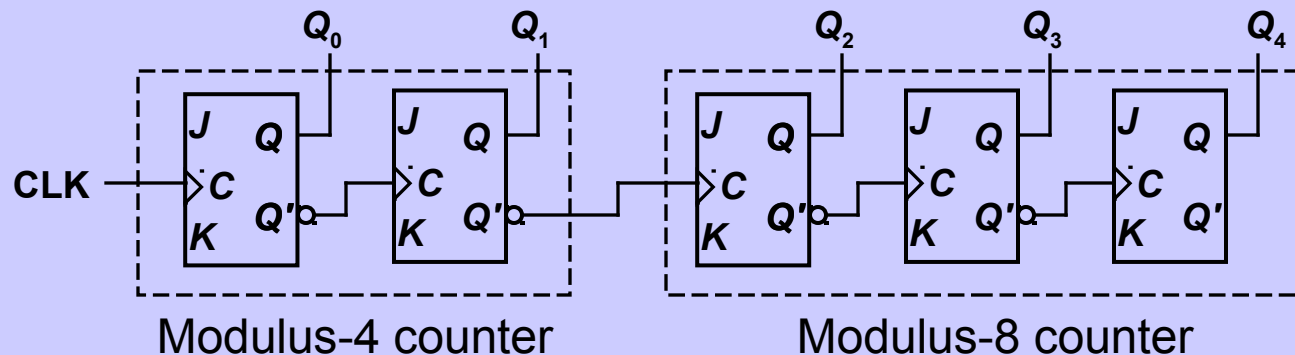- Larger asynchronous (ripple) counter can be constructed by cascading smaller ripple counters.
- Connect last-stage output of one counter to the clock input of next counter so as to achieve higher-modulus operation.
- Example: A modulus-32 ripple counter constructed from a modulus-4 counter and a modulus-8 counter.



Cascading Asynchronous Counters

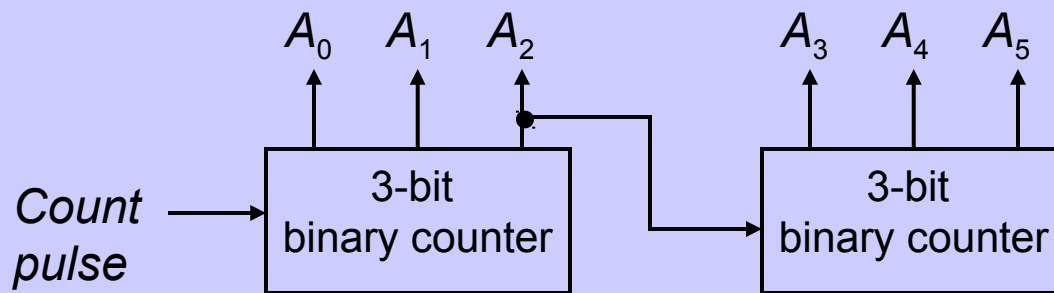- Example: A 6-bit binary counter (counts from 0 to 63) constructed from two 3-bit counters.




A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	0
0	0	0	0	0	1
0	0	0	:	:	:
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	0	1
:	:	:	:	:	:

Simple Registers

Cascading Asynchronous Counters

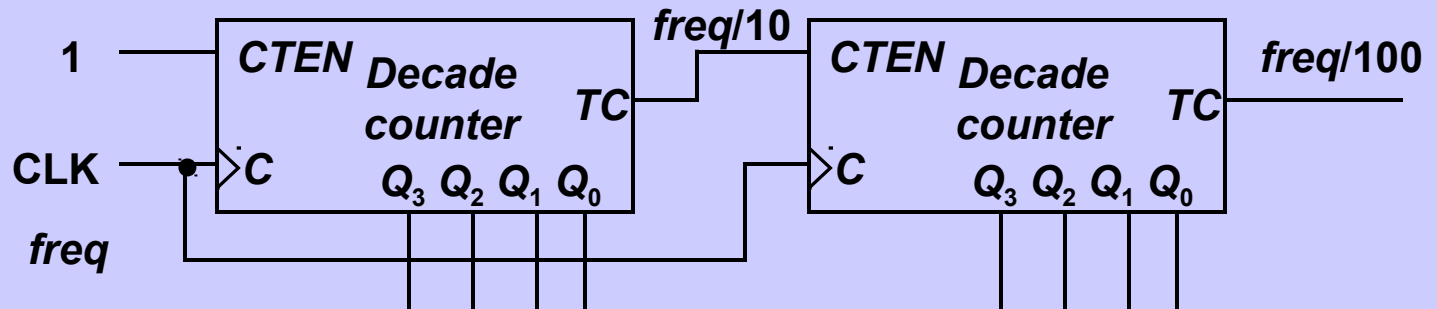
- If counter is not a binary counter, requires additional output.
- Example: A modulus-100 counter using two decade counters.



$TC = 1$ when counter recycles to 0000

Synchronous (Parallel) Counters

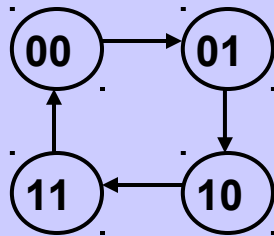- **Synchronous (parallel) counters:** the flip-flops are clocked at the same time by a common clock pulse.
- We can design these counters using the sequential logic design process (covered in Lecture #12).
- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).



Present state		Next state		Flip-flop inputs	
A_1	A_0	A_1^+	A_0^+	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1


Synchronous (Parallel) Counters

- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).

Present state		Next state		Flip-flop inputs	
A_1	A_0	A_1^+	A_0^+	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

$$TA_1 = A_0$$


$$TA_0 = 1$$

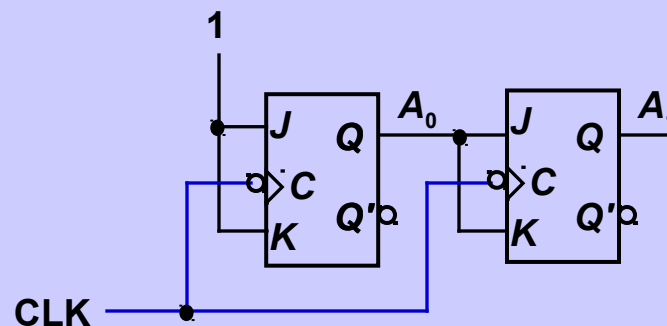


Synchronous (Parallel) Counters

- Example: 3-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J, K inputs).


Present state			Next state			Flip-flop inputs		
A_2	A_1	A_0	A_2^+	A_1^+	A_0^+	TA_2	TA_1	TA_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

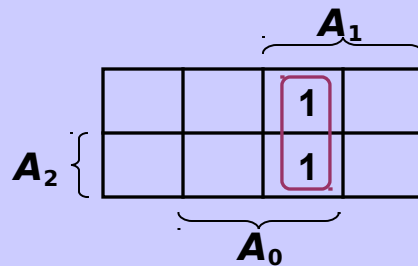

$$TA_2 = A_1 \cdot A_0$$

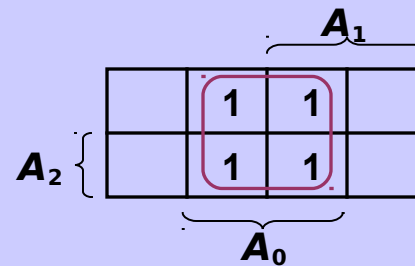

$$TA_1 = A_0$$

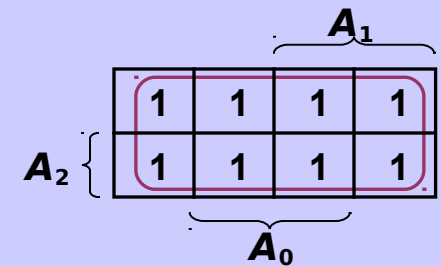

$$TA_0 = 1$$


Simple Registers

- Example: 3-bit synchronous binary counter (cont'd).

$$TA_2 = A_1.A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

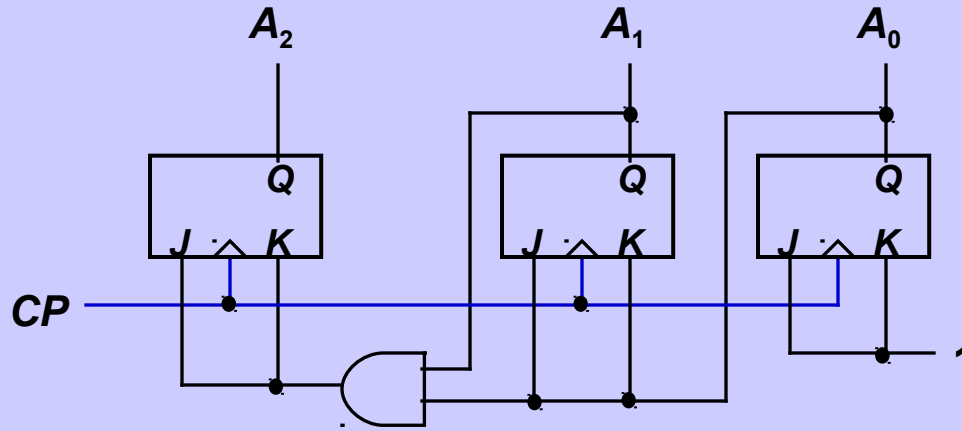

Synchronous (Parallel) Counters

- Note that in a binary counter, the n^{th} bit (shown underlined) is always complemented whenever

$$\underline{0}11\dots11 \rightarrow \underline{1}00\dots00$$

$$\text{or } \underline{1}11\dots11 \rightarrow \underline{0}00\dots00$$

- Hence, X_n is complemented whenever

$$X_{n-1}X_{n-2} \dots X_1X_0 = 11\dots11.$$

- As a result, if T flip-flops are used, then

$$TX_n = X_{n-1} \cdot X_{n-2} \cdot \dots \cdot X_1 \cdot X_0$$

Synchronous (Parallel) Counters


- Example: 4-bit synchronous binary counter.

$$TA_3 = A_2 \cdot A_1 \cdot A_0$$

$$TA_2 = A_1 \cdot A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

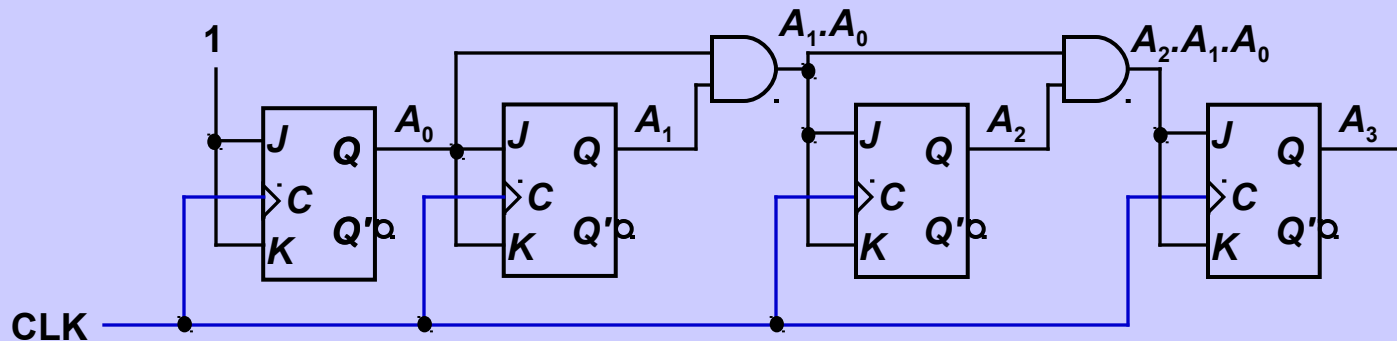

Synchronous (Parallel) Counters

- Example: Synchronous decade/BCD counter.

Clock pulse	Q_3	Q_2	Q_1	Q_0
Initially	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10 (recycle)	0	0	0	0

$$T_0 = 1$$

$$T_1 = Q_3' \cdot Q_0$$

$$T_2 = Q_1 \cdot Q_0$$

$$T_3 = Q_2 \cdot Q_1 \cdot Q_0 + Q_3 \cdot Q_0$$


- Example: Synchronous decade/BCD counter (cont'd).

$$T_0 = 1$$

$$T_1 = Q_3' \cdot Q_0$$

$$T_2 = Q_1 \cdot Q_0$$

$$T_3 = Q_2.Q_1.Q_0 + Q_3.Q_0$$

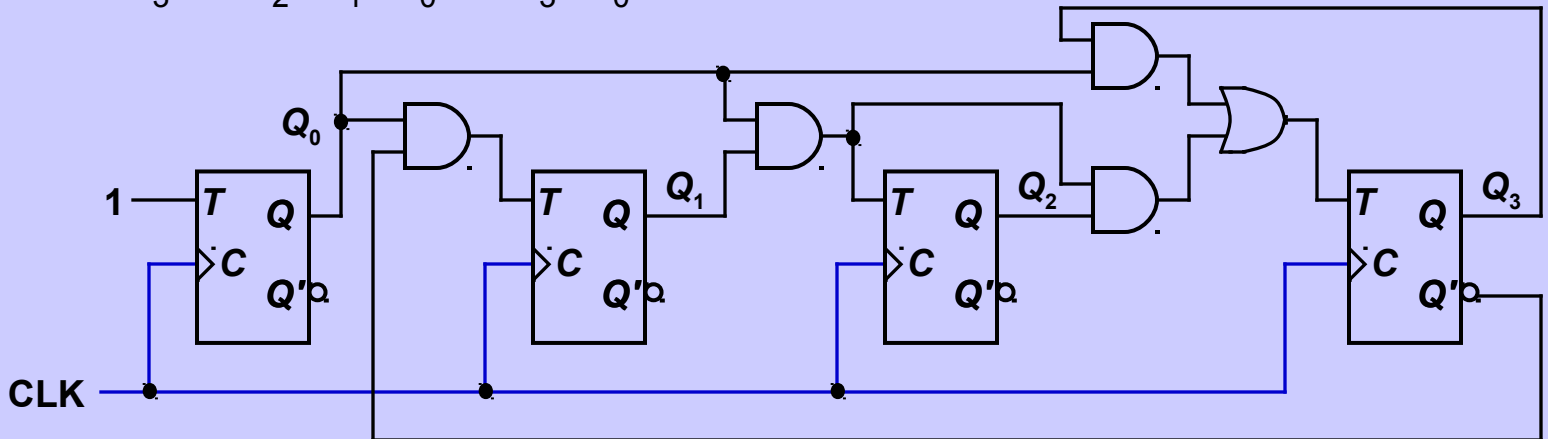

Up/Down Synchronous Counters

- Up/down synchronous counter: a *bidirectional* counter that is capable of counting either up or down.
- An input (control) line $\overline{Up/Down}$ (or simply \overline{Up}) specifies the direction of counting.
 - ❖ $\overline{Up/Down} = 1 \rightarrow$ Count upward
 - ❖ $\overline{Up/Down} = 0 \rightarrow$ Count downward

Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter.

Clock pulse	<i>Up</i>	Q_2	Q_1	Q_0	<i>Down</i>
0	↻	0	0	0	↻
1	↻	0	0	1	↻
2	↻	0	1	0	↻
3	↻	0	1	1	↻
4	↻	1	0	0	↻
5	↻	1	0	1	↻
6	↻	1	1	0	↻
7	↻	1	1	1	↻

$$TQ_0 = 1$$

$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$

$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$

Up counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0$$

$$TQ_2 = Q_0 \cdot Q_1$$

Down counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0'$$

$$TQ_2 = Q_0' \cdot Q_1'$$


Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter (cont'd).

$$TQ_0 = 1$$


$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$
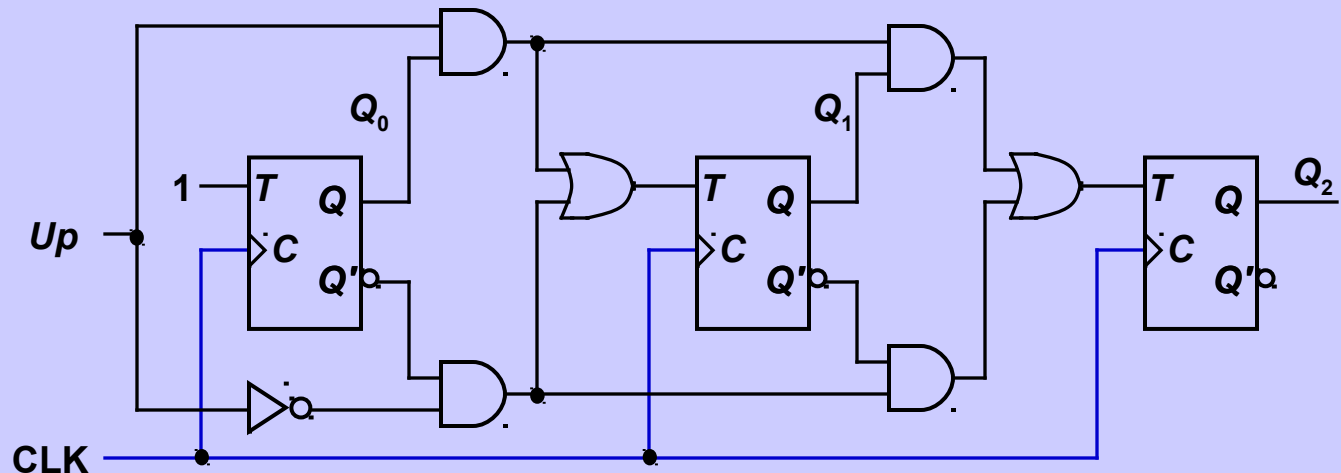
$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$



Designing Synchronous Counters

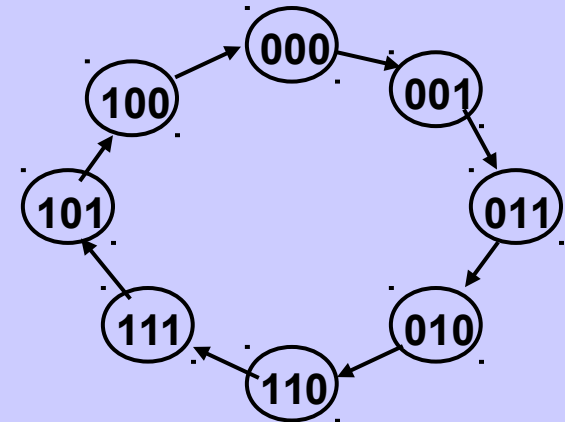- Covered in Lecture #12.
- Example: A 3-bit Gray code counter (using JK flip-flops).



Present state			Next state			Flip-flop inputs					
Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+	JQ_2	KQ_2	JQ_1	KQ_1	JQ_0	KQ_0
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	1	0	X	1	X	X	0
0	1	0	1	1	0	1	X	X	0	0	X
0	1	1	0	1	0	0	X	X	0	X	1
1	0	0	0	0	0	X	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	1	0	1	X	0	X	1	X	0

Designing Synchronous Counters

- 3-bit Gray code counter: flip-flop inputs.

		Q_1Q_0			
Q_2		00	01	11	10
	0				1
	1	X	X	X	X

$JQ_2 = Q_1 \cdot Q_0'$

		Q_1Q_0			
Q_2		00	01	11	10
	0	X	X	X	X
	1	1			

$KQ_2 = Q_1' \cdot Q_0'$

		Q_1Q_0			
Q_2		00	01	11	10
	0		1	X	X
	1			X	X

$JQ_1 = Q_2' \cdot Q_0$

		Q_1Q_0			
Q_2		00	01	11	10
	0	X	X		
	1	X	X	1	

$KQ_1 = Q_2 \cdot Q_0$

		Q_1Q_0			
Q_2		00	01	11	10
	0	1	X	X	
	1		X	X	1

$JQ_0 = Q_2' \cdot Q_1 + Q_2' \cdot Q_1'$
 $= (Q_2 \oplus Q_1)'$

		Q_1Q_0			
Q_2		00	01	11	10
	0	X		1	X
	1	X	1		X

$KQ_0 = Q_2 \cdot Q_1' + Q_2' \cdot Q_1$
 $= Q_2 \oplus Q_1$

Designing Synchronous Counters

- 3-bit Gray code counter: logic diagram.

$$JQ_2 = Q_1 \cdot Q_0'$$


$$KQ_2 = Q_1' \cdot Q_0'$$

$$JQ_1 = Q_2' \cdot Q_0$$

$$KQ_1 = Q_2 \cdot Q_0$$

$$JQ_0 = (Q_2 \oplus Q_1)'$$

$$KQ_0 = Q_2 \oplus Q_1$$

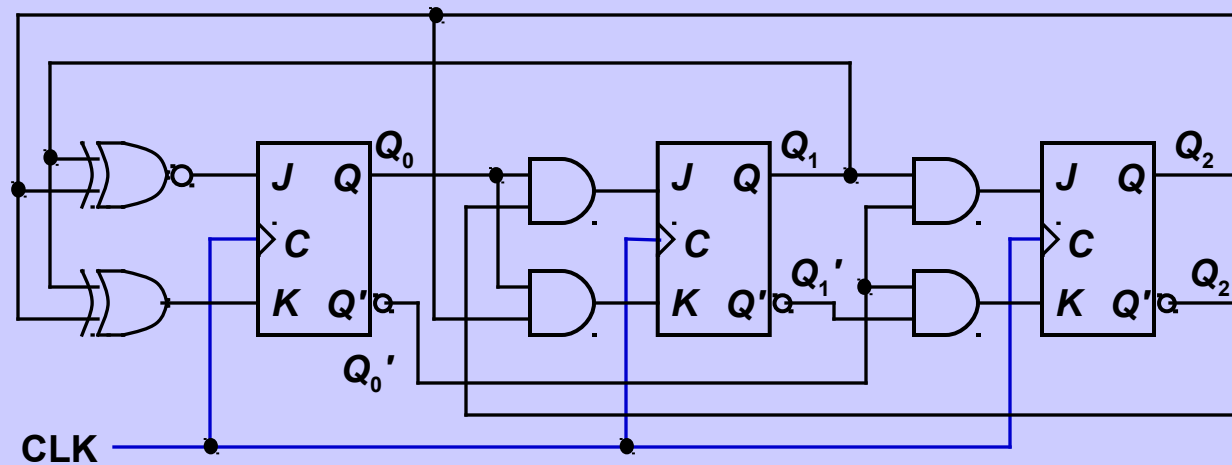


Decoding A Counter

- **Decoding a counter** involves determining which state in the sequence the counter is in.
- Differentiate between *active-HIGH* and *active-LOW* decoding.
- Active-HIGH decoding: output HIGH if the counter is in the state concerned.
- Active-LOW decoding: output LOW if the counter is in the state concerned.


Decoding A Counter

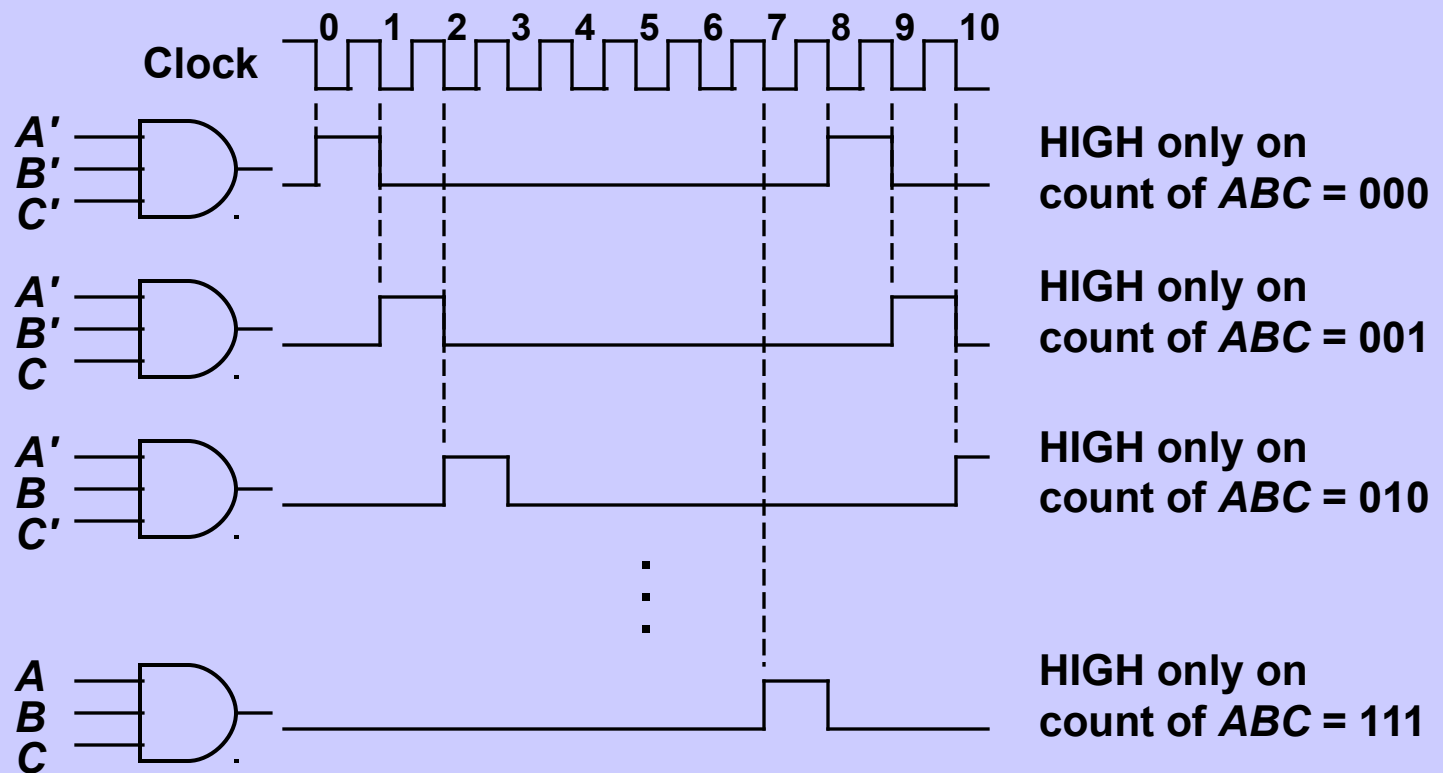- Example: MOD-8 ripple counter (active-HIGH decoding).




Decoding A Counter

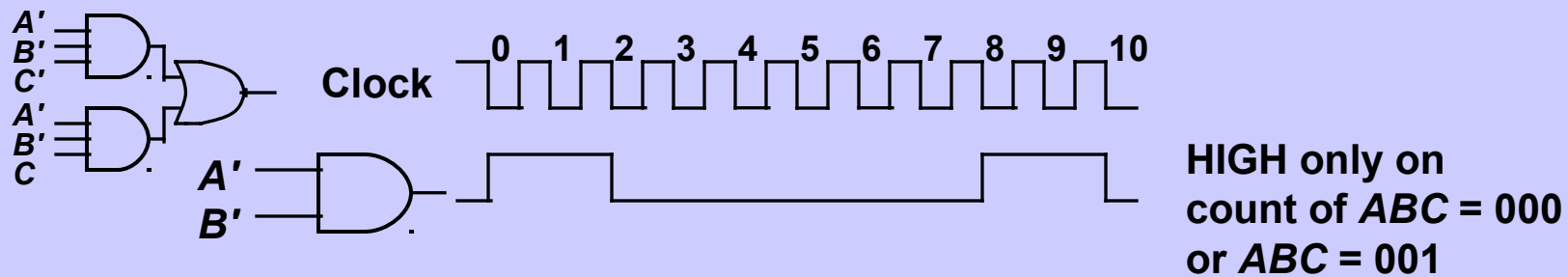- Example: To detect that a MOD-8 counter is in state 0 (000) or state 1 (001).



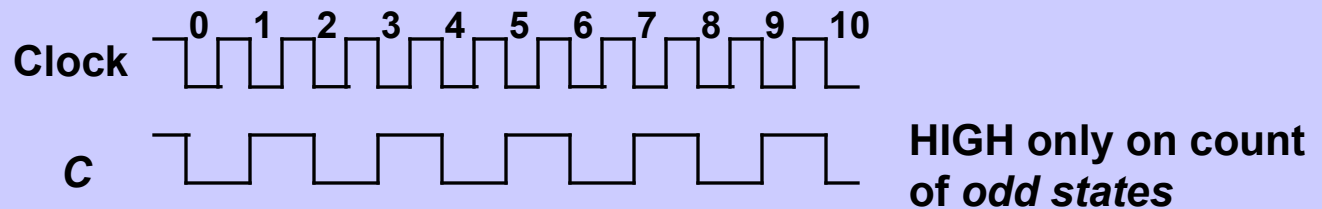- Example: To detect that a MOD-8 counter is in the odd states (states 1, 3, 5 or 7), simply use C .







Counters with Parallel Load

- Counters could be augmented with parallel load capability for the following purposes:
 - ❖ To start at a different state
 - ❖ To count a different sequence
 - ❖ As more sophisticated register with increment/decrement functionality.



Counters with Parallel Load

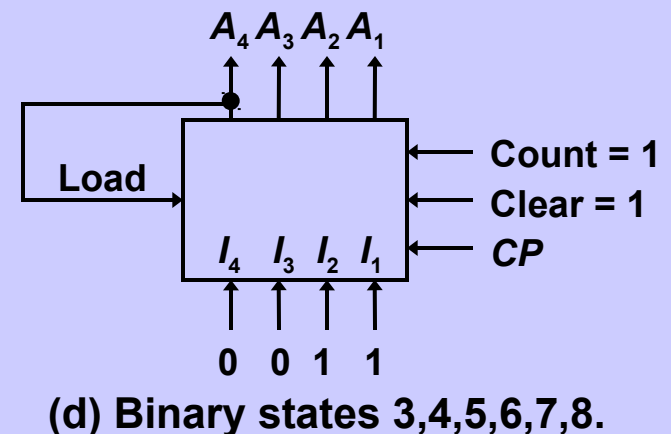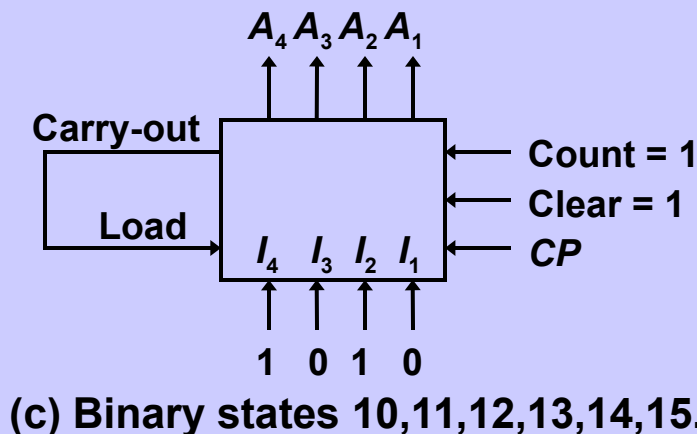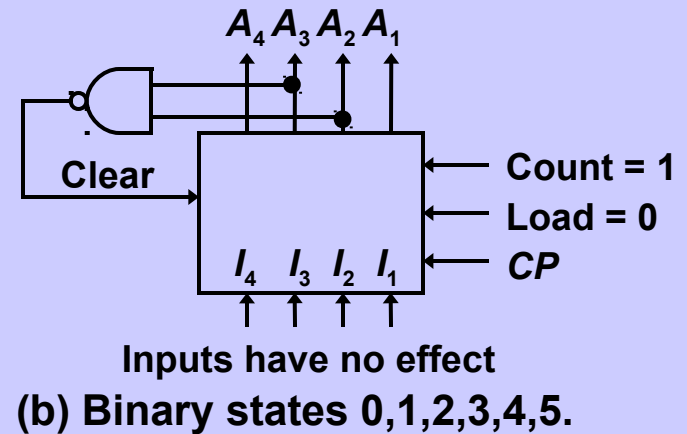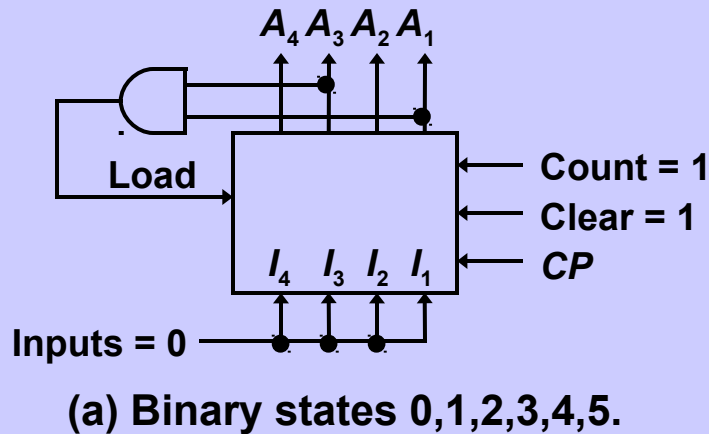
- Different ways of getting a MOD-6 counter:



Counters with Parallel Load

- 4-bit counter with parallel load.

Clear	CP	Load	Count	Function
0	X	X	X	Clear to 0
1	X	0	0	No change
1	↑	1	X	Load inputs
1	↑	0	1	Next state

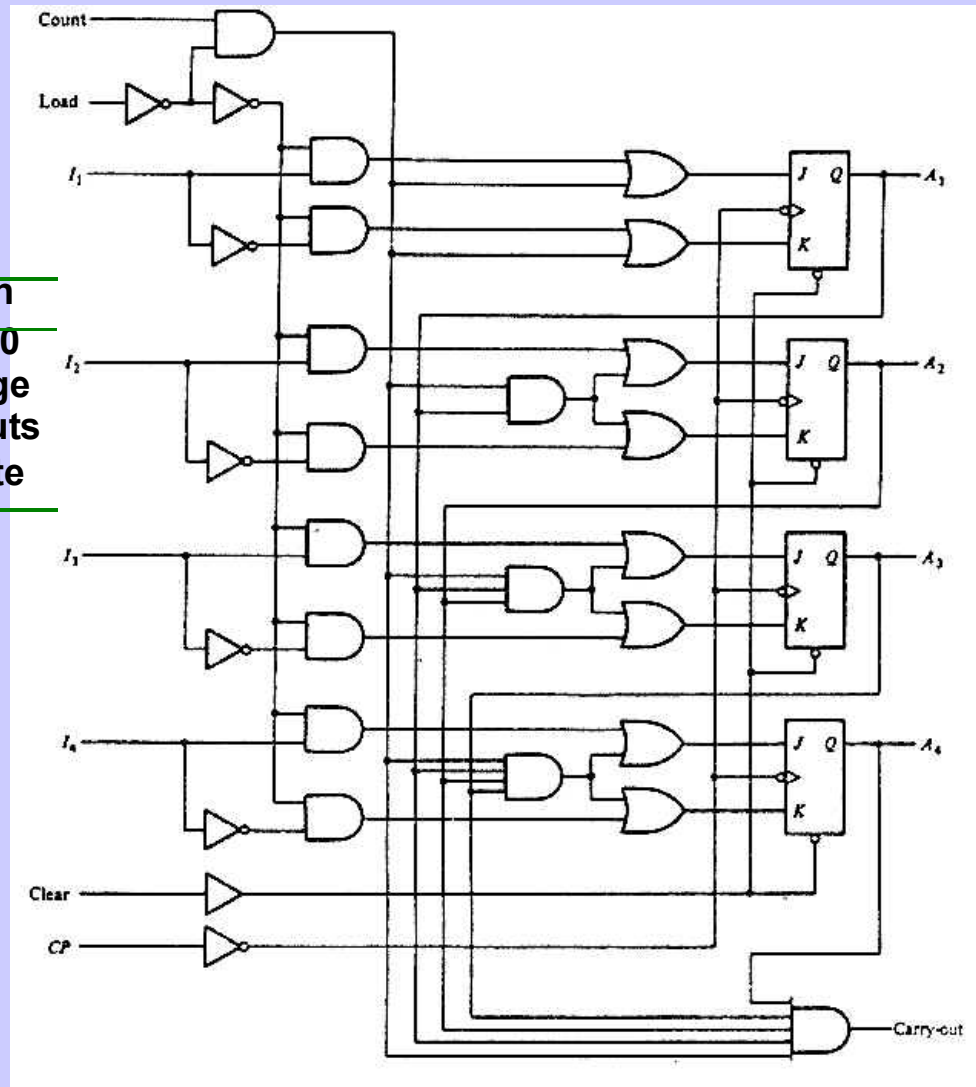

Shift Register Counters

- **Shift register counter**: a shift register with the serial output connected back to the serial input.
- They are classified as counters because they give a specified sequence of states.
- Two common types: the *Johnson counter* and the *Ring counter*.


Ring Counters

- One flip-flop (stage) for each state in the sequence.
- The output of the last stage is connected to the D input of the first stage.
- An n -bit ring counter cycles through n states.
- No decoding gates are required, as there is an output that corresponds to every state the counter is in.




Ring Counters

- Example: A 6-bit (MOD-6) ring counter.

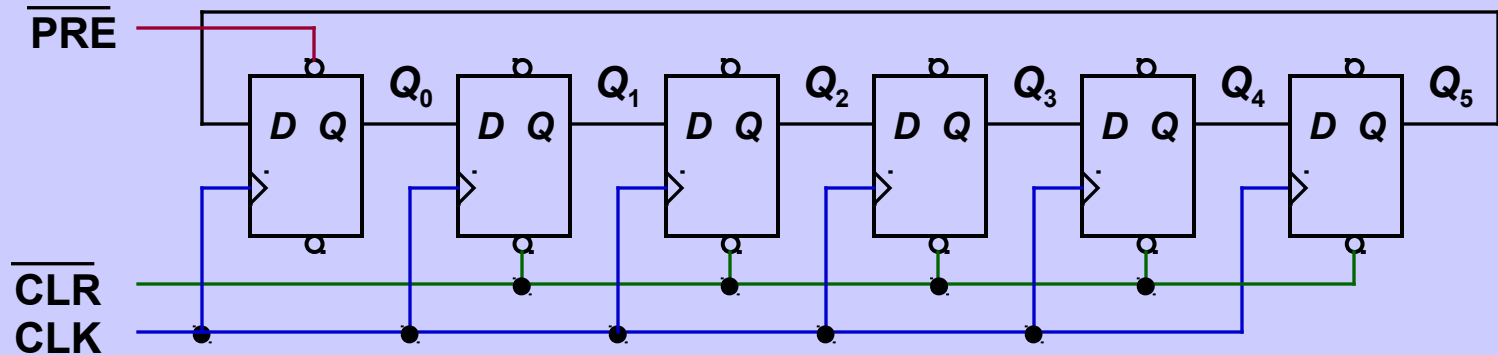

Clock	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅
0	1	0	0	0	0	0
1	0	1	0	0	0	0
2	0	0	1	0	0	0
3	0	0	0	1	0	0
4	0	0	0	0	1	0
5	0	0	0	0	0	1

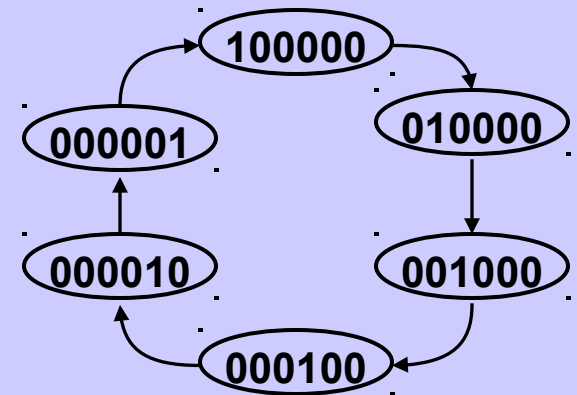


Johnson Counters


- The complement of the output of the last stage is connected back to the D input of the first stage.
- Also called the *twisted-ring counter*.
- Require fewer flip-flops than ring counters but more flip-flops than binary counters.
- An n -bit Johnson counter cycles through $2n$ states.
- Require more decoding circuitry than ring counter but less than binary counters.

Johnson Counters

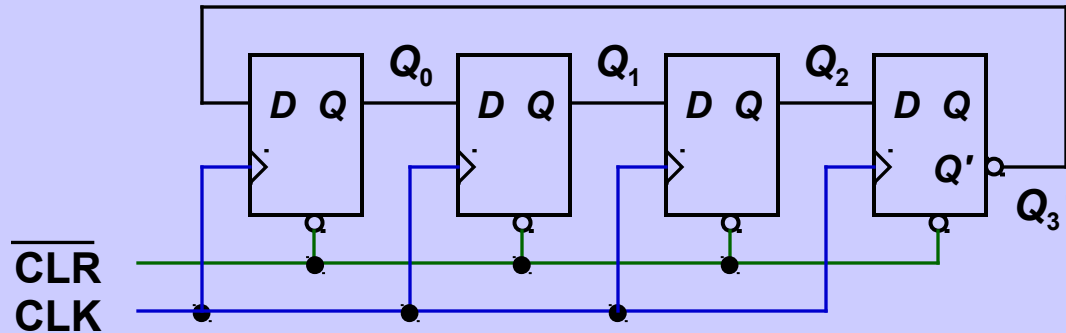- Example: A 4-bit (MOD-8) Johnson counter.











Clock	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

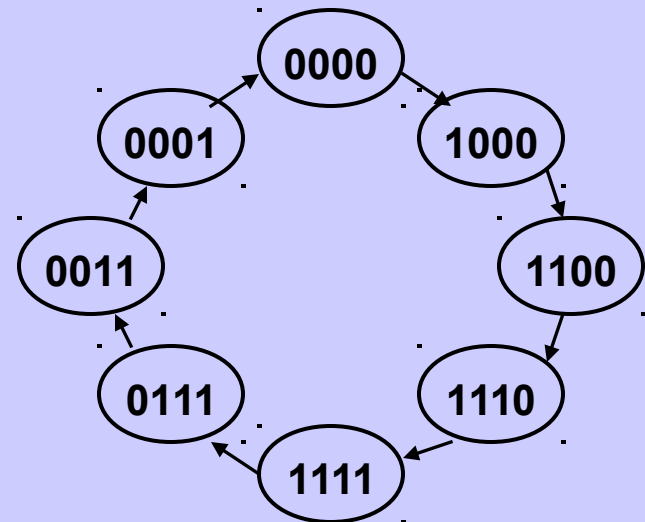

Johnson Counters

- Decoding logic for a 4-bit Johnson counter.

Clock	A	B	C	D	Decoding
0	0	0	0	0	$A'.D'$
1	1	0	0	0	$A.B'$
2	1	1	0	0	$B.C'$
3	1	1	1	0	$C.D'$
4	1	1	1	1	$A.D$
5	0	1	1	1	$A'.B$
6	0	0	1	1	$B'.C$
7	0	0	0	1	$C'.D$

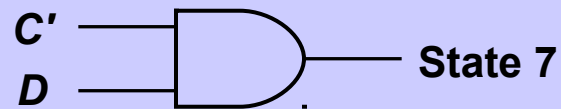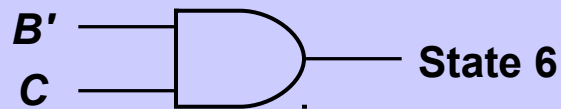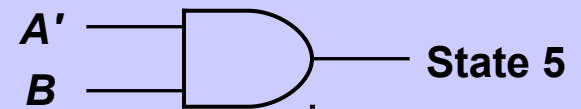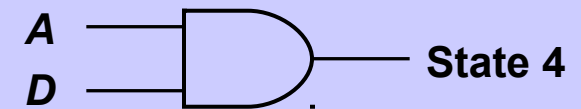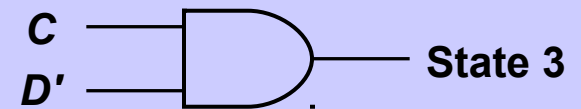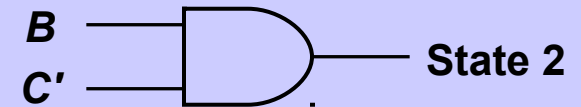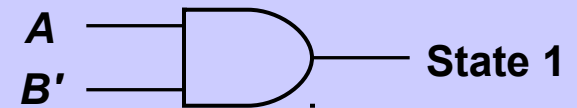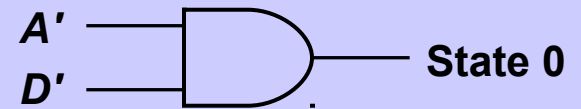


Random Access Memory (RAM)

- A memory unit stores binary information in groups of bits called *words*.
- The data consists of n lines (for n -bit words). **Data input lines** provide the information to be stored (*written*) into the memory, while **data output lines** carry the information out (*read*) from the memory.
- The **address** consists of k lines which specify which word (among the 2^k words available) to be selected for reading or writing.
- The control lines **Read** and **Write** (usually combined into a single control line *Read/Write*) specifies the direction of transfer of the data.

Random Access Memory (RAM)

- Block diagram of a memory unit:

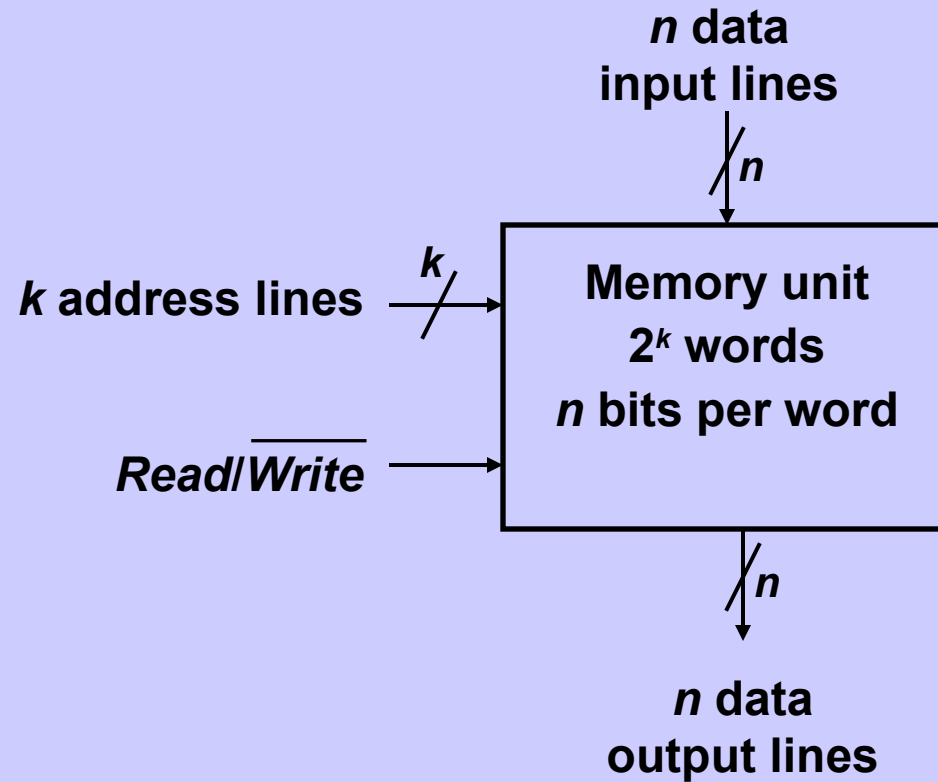

Random Access Memory (RAM)

- Content of a 1024 x 16-bit memory:

Memory address		Memory content
binary	decimal	
0000000000	0	1011010111011101
0000000001	1	1010000110000110
0000000010	2	0010011101110001
:	:	:
:	:	:
1111111101	1021	1110010101010010
1111111110	1022	0011111010101110
1111111111	1023	1011000110010101

Random Access Memory (RAM)

■ The **Write** operation:

- ❖ Transfers the address of the desired word to the address lines
- ❖ Transfers the data bits (the word) to be stored in memory to the data input lines
- ❖ Activates the *Write* control line (set *Read/Write* to 0)

■ The **Read** operation:

- ❖ Transfers the address of the desired word to the address lines
- ❖ Activates the *Read* control line (set *Read/Write* to 1)

Random Access Memory (RAM)


- The Read/Write operation:

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word


- Two types of RAM: Static and dynamic.
 - ❖ Static RAMs use flip-flops as the memory cells.
 - ❖ Dynamic RAMs use capacitor charges to represent data. Though simpler in circuitry, they have to be constantly refreshed.

Random Access Memory (RAM)

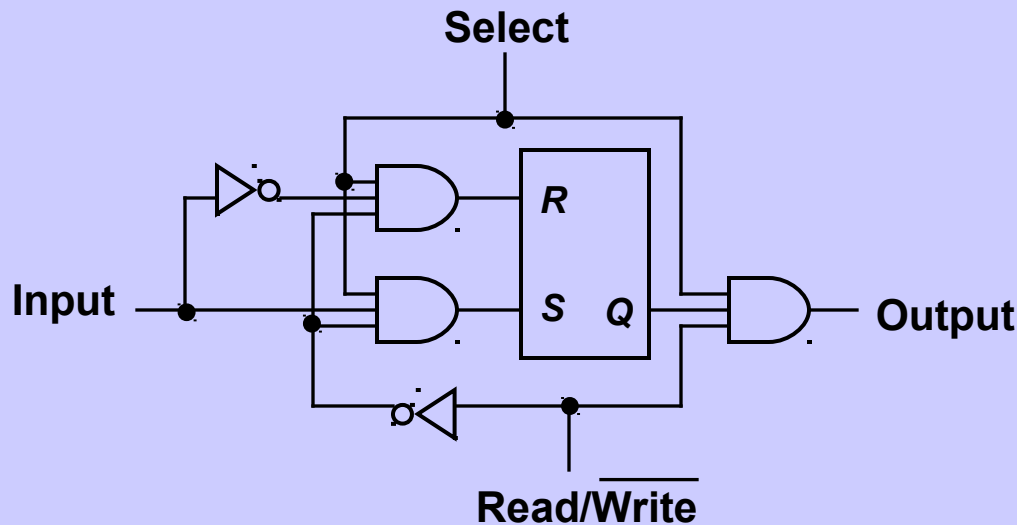- A single memory cell of the static RAM has the following logic and block diagrams.




Logic diagram

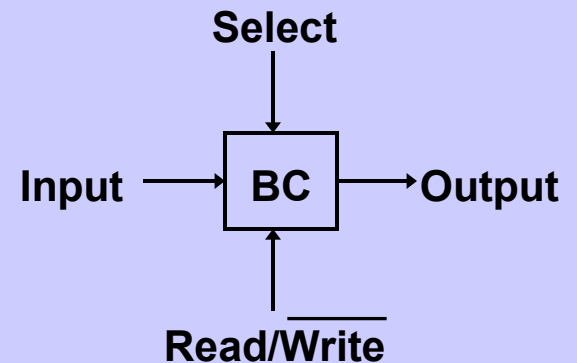

Block diagram


Random Access Memory (RAM)

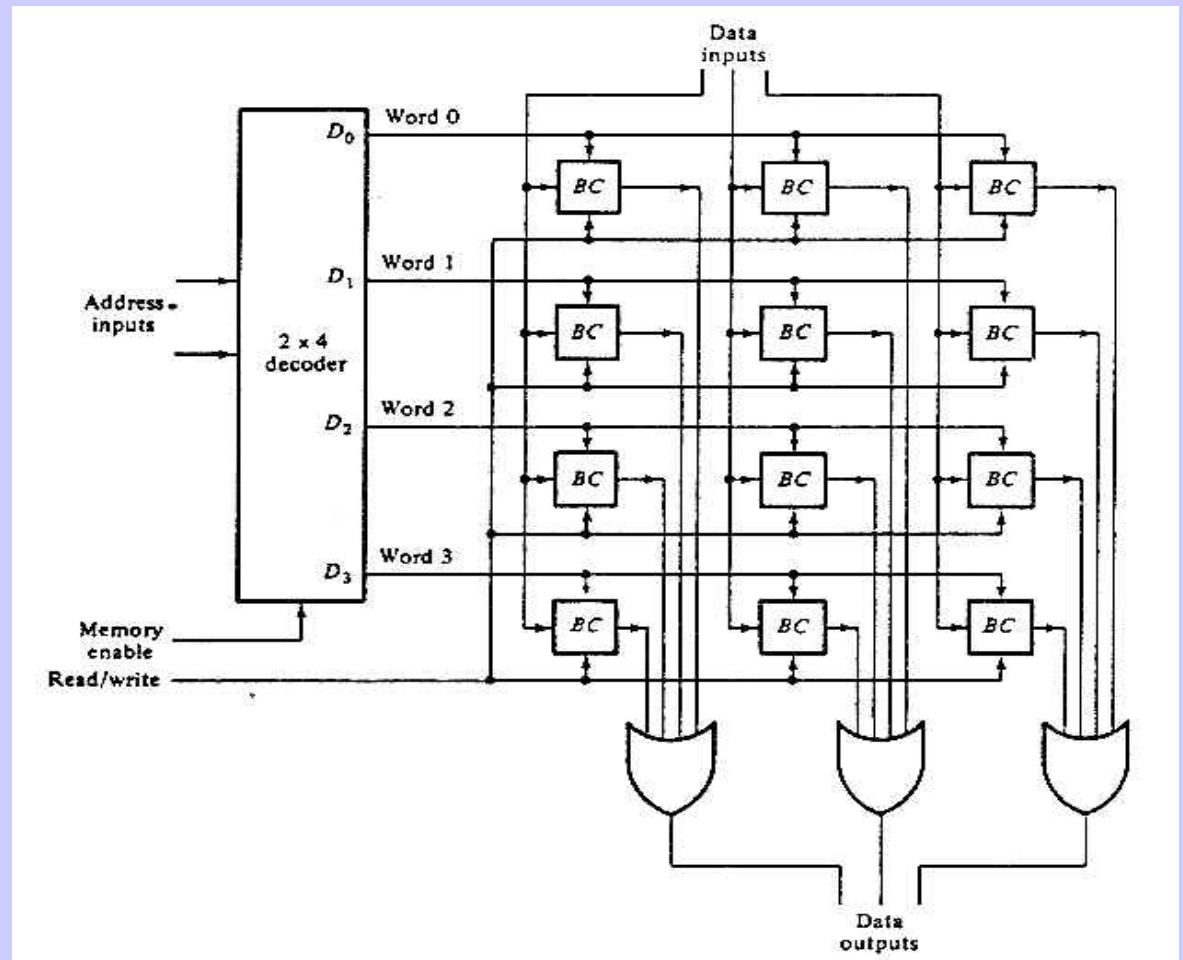- Logic construction of a 4 x 3 RAM (with decoder and OR gates):




Random Access Memory (RAM)

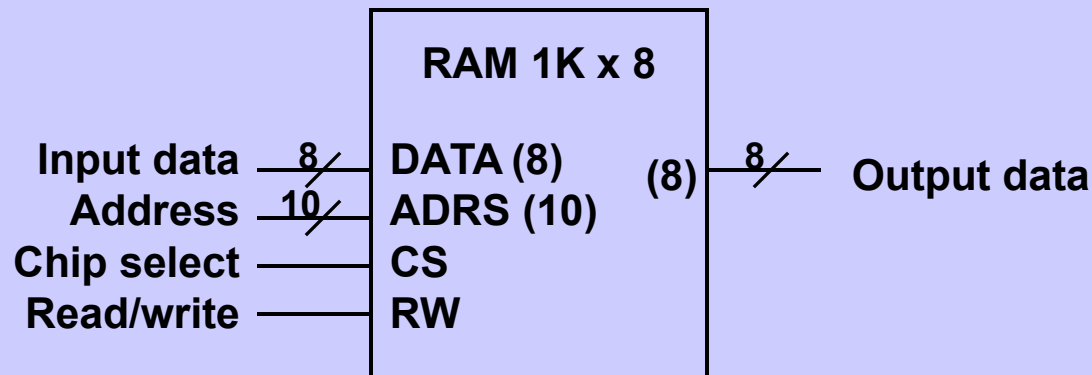- An array of RAM chips: memory chips are combined to form larger memory.
- A 1K x 8-bit RAM chip:



Block diagram of a 1K x 8 RAM chip

Random Access Memory (RAM)

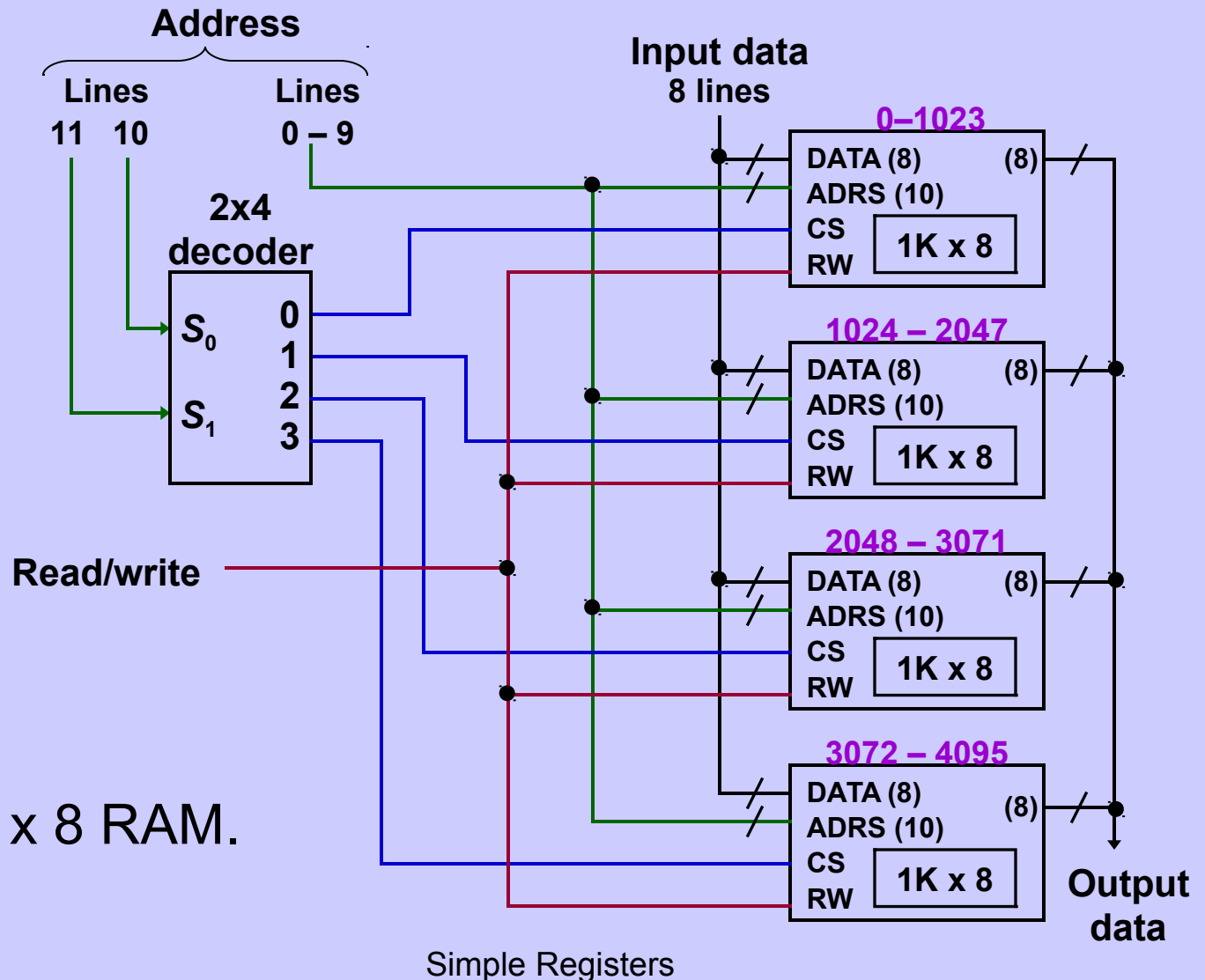

- 4K x 8 RAM.



End of segment